

DN68 ZXSC310 High power torch reference design

Description

This design note shows a typical ZXSC310 LED driver circuit for a high powered LED torch. The input voltage ranges from 0.7V to 1.6V with a maximum output current of 335mA at 1.4V input.

A typical schematic diagram is shown in Figure 1.


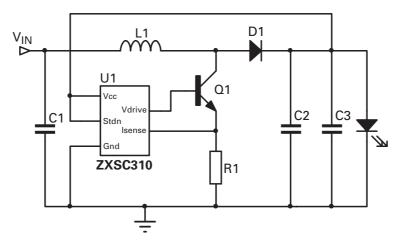


Figure 1 Schematic diagram

Reference	Value	Part number	Manufacturer	Contact details	Comments
U1		ZXSC310E5	Zetex	www.zetex.com	LED driver in SOT23-5
Q1		FMMT617	Zetex	www.zetex.com	Low sat. NPN in SOT23
D1	2A	ZHCS2000	Zetex	www.zetex.com	2A Schottky in SOT23
L1	7.5µH	DO3316P-153x2	Coilcraft	www.coilcraft.com	I _{SAT} = 3A
R1	19.5m Ω	Generic	Generic	NA	0805 size
C1	1μF	Generic	Generic	NA	
C2	220μF	Generic	Generic	NA	
C3	100μF	Generic	Generic	NA	

Table 1Bill of materials

DN68

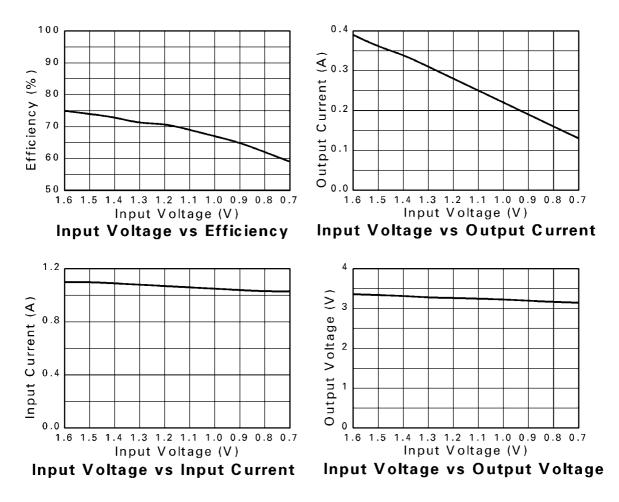



Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH	Zetex Inc	Zetex (Asia Ltd)	Zetex Semiconductors plc
Streitfeldstraße 19	700 Veterans Memorial Highway	3701-04 Metroplaza Tower 1	Zetex Technology Park, Chaddertor
D-81673 München	Hauppauge, NY 11788	Hing Fong Road, Kwai Fong	Oldham, OL9 9LL
Germany	USA	Hong Kong	United Kingdom
Telefon: (49) 89 45 49 49 0	Telephone: (1) 631 360 2222	Telephone: (852) 26100 611	Telephone: (44) 161 622 4444
Fax: (49) 89 45 49 49 49	Fax: (1) 631 360 8222	Fax: (852) 24250 494	Fax: (44) 161 622 4446
europe.sales@zetex.com	usa.sales@zetex.com	asia.sales@zetex.com	hq@zetex.com

For international sales offices visit www.zetex.com/offices

Zetex products are distributed worldwide. For details, see www.zetex.com/salesnetwork

This publication is issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contact or be regarded as a representation relating to the products or services concerned. The company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.