

LED Driver Design with iW1678
(AC Input 180V–264V_{AC}, Output 10 LEDs)

LED Driver Design with iW1678 (AC Input 180–264V_{AC}, Output 10 LEDs) EBC883

1.0. Introduction	3
2.0. Design Features	3
3.0. Design Specification	4
4.0. Schematic	5
5.0. PCB Layout.....	5
6.0. Bill Of Materials.....	6
7.0. Transformer Drawing	7
8.0. Performance	8
8.1. Constant Current and Efficiency	8
8.2. Current Harmonics	8
8.3. Conducted EMI	9

1.0 Introduction

This reference design describes a 10 LEDs output, high line input (180–264V_{AC}) power supply for non-dimmable LED applications. For this design the iW1678-00 is used. This document contains the complete specification of the LED driver, a detailed circuit diagram, an entire bill of materials required to build the LED driver, a drawing of the power transformer, and test data of the most important performance.


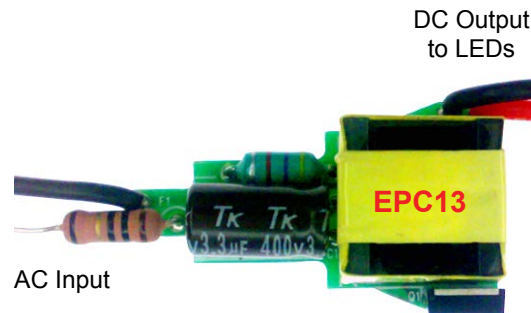


Figure 1.1 PCB Top View

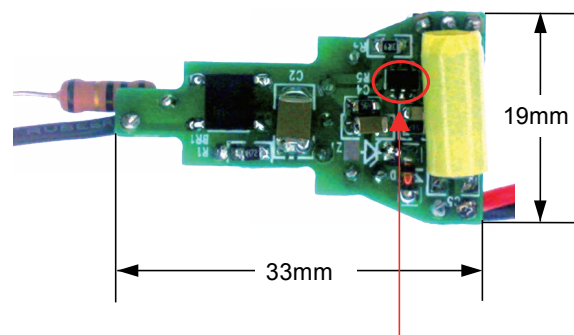

iW1678-00 Digital & Primary VMS Controller
(SOT23-5 Package)

Figure 1.2 PCB Bottom View

2.0 Design Features

- For candle LED lamp
- AC input range 180-264V_{AC}
- Output 10 LEDs at 160mA
- Non-isolated applications
- High efficiency and minimum parts count
- Meet EMI EN55015B-QP limits

3.0 Design Specification

The information in the table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment
Input						
Voltage	V_{IN}	180	230	264	V _{AC}	2 wire
Frequency	f_{LINE}		50		Hz	
Output						
Constant output voltage	V_{OUT_CV}		32		V	Measured at end of PCB
Constant output current	I_{OUT_CC}		160		mA	
Total Output Power						
Continuous output power	P_{OUT}		5		W	
Efficiency	η		86		%	Measured at end of PCB, V _{IN} =230V _{AC} (T _{AMB} =25°C)
Power factor	PF		0.5			Harmonic meet IEC61000-3-2
Environmental						
Conducted EMI		Meets EN55015B				
Operation temperature	T_{OPR}		40		°C	Free convection, sea level

4.0 Schematic


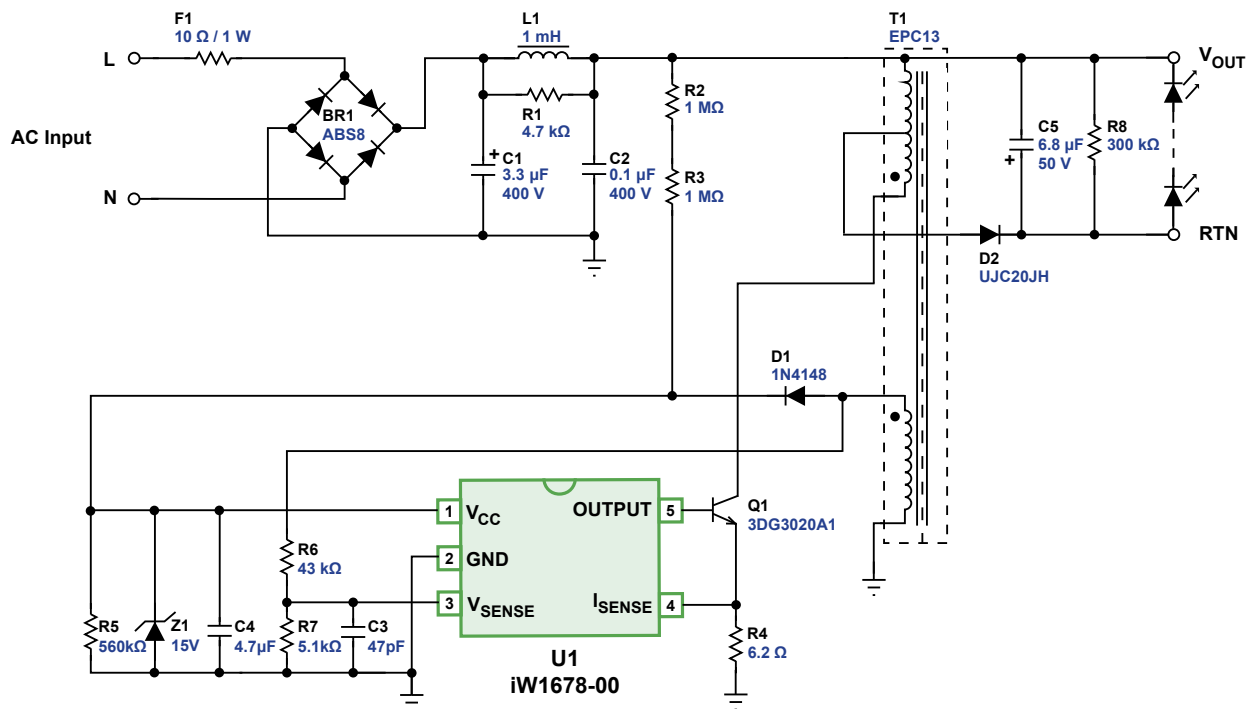


Figure 4.1 Design Schematic

5.0 PCB Layout

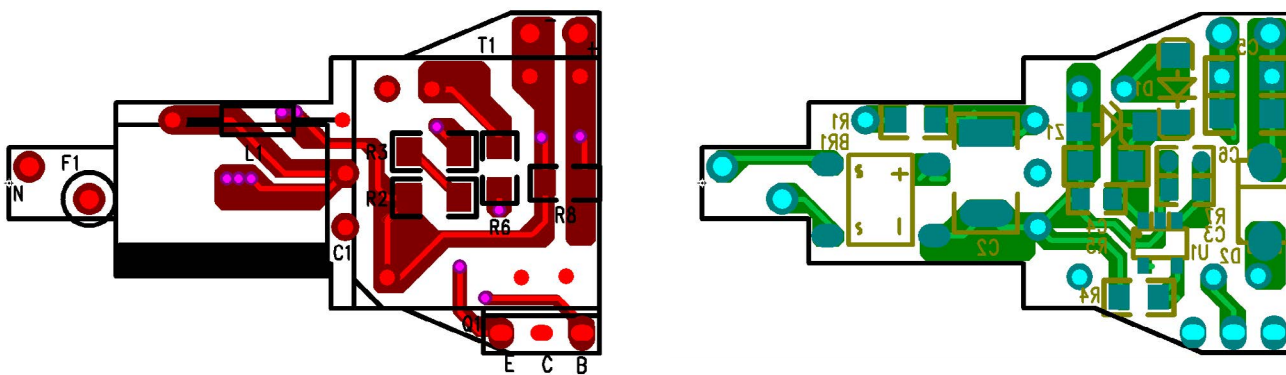

PCB Top

PCB Bottom


Figure 5.1 PCB Layout 33.0 mm x 19.0 mm

6.0 Bill of Materials

Item	Qty.	Ref.	Description	Manufacturer P/N	Manufacturer
1	1	U1	iW1678-00, off-line digital & primary VMS controller, SOT23-5	iW1678-00	iWatt, Inc
2	1	C1	3.3μF, 400V, E-CAP, (Φ6.3mm×11.5mm)	2GUTWHS3R3M0E12	TOSHIN KOGYO Co.
3	1	C2	0.1μF, 400V, CBB, P=5.5mm	MTF400V	Carli
4	1	C3	47pF, 50V, X7R, SMD-0603	06035C470KAT2A	AVX Corporation
5	1	C4	4.7μF, 25V, X7R, SMD-1206	CGA5L1X7R1E475K	TDK Corporation
6	1	C5	6.8μF, 50V, E-CAP, (Φ6.3mm×11.5mm)	KLH-050V6R8ME110	KOSHIN
7	1	R1	4.7KΩ ±5%, SMD-0805	ERJ-6GEYJ472V	Panasonic - ECG
8	2	R2, R3	1MΩ ±5%, SMD-1206	ERJ-8GEYJ105V	Panasonic - ECG
9	1	R4	3.9Ω ±5%, SMD-0805	ERJ-6GEYJ3R9V	Panasonic - ECG
10	1	R5	560KΩ ±5%, SMD-0805	ERJ-6GEYJ564V	Panasonic - ECG
11	1	R6	43KΩ ±1%, SMD-0805	ERJ-6ENF4302V	Panasonic - ECG
12	1	R7	5.1KΩ ±1%, SMD-0805	ERJ-6ENF5101V	Panasonic - ECG
13	1	R8	300KΩ ±5%, SMD-0805	ERJ-6GEYJ304V	Panasonic - ECG
14	1	BR1	1A, 800V, bridge rectifier, ABS	ABS8	Taiwan Semiconductor
15	1	D1	150MA, 75V, rectifier, SOD323F	1N4148WS	Fairchild Semiconductor
16	1	D2	2A, 200V, schottky diode, DO-214AC (SMA)	SM2200A	Eris Technology
17	1	Z1	Zener, 15V, SOD-323	BZT52C15S-7-F	Diodes Inc
18	1	F1	10Ω, fusible resistor, 1W	FRM1WJT-52-10R	Yageo
19	1	L1	1mH, filter inductor, Axial	8230-92-RC	Bourns Inc.
20	1	Q1	1.5A, 450V, NPN transistor, TO-251	3DD3020A1	HuaJing Mirco Co., Ltd
21	1	T1	EPC13, Horizontal	CUSTOM	

7.0 Transformer Drawing

Schematic:

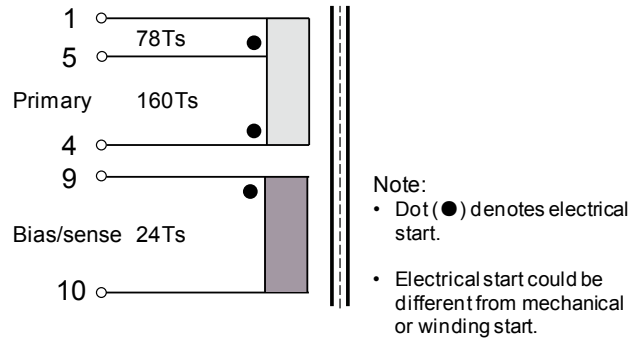

Electrical Specifications:

1. Primary inductance (L_p) = 3.2mH @10KHz
2. Primary leakage inductance (L_k) < 20 μ H @10KHz
3. Electrical strength = 3KV, 50/60Hz, 1min.

Materials:

1. Core: EPC13 (ferrite material TDK PC40 or equivalent)
2. Bobbin: EPC13 Horizontal. Primary=5, Secondary=5
3. Magnet wires (pri): type 2-UEW
4. Layer insulation tape: 3M1298 or equivalent

Finished:

1. Cut remained of pin 2,3,6,7,8
2. Varnish the complete assembly

8.0 Performance

8.1 Constant Current and Efficiency

V _{IN} (V _{AC})	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	η (%)	Power Factor
180	5.66	31.47	0.154	85.63%	0.606
190	5.64	31.43	0.154	85.82%	0.596
200	5.62	31.41	0.154	86.07%	0.589
210	5.61	31.39	0.154	86.17%	0.581
220	5.61	31.38	0.154	86.14%	0.573
230	5.60	31.37	0.154	86.27%	0.573
240	5.59	31.35	0.154	86.37%	0.559
250	5.59	31.34	0.154	86.06%	0.553
260	5.58	31.32	0.154	86.16%	0.546
264	5.58	31.31	0.153	85.85%	0.544

8.2 Current Harmonics

Current Harmonics

THD=152.42 % (PF=0.514) PASSED P< 25 u

No	%	Lim %	No	%	Lim %	No	%	Lim %
1	100.00		15	20.95		29	11.05	
2	0.17		16	0.35		30	0.21	
3	91.94		17	20.16		31	9.81	
4	0.17		18	0.48		32	0.21	
5	77.38		19	17.80		33	9.01	
6	0.13		20	0.44		34	0.29	
7	59.08		21	14.77		35	0.77	
8	0.21		22	0.30		36	0.31	
9	41.10		23	12.98		37	0.66	
10	0.28		24	0.27		38	0.28	
11	27.69		25	12.37		39	0.29	
12	0.28		26	0.21		40	0.24	
13	21.79		27	12.10				
14	0.26		28	0.23				

Current range: 0.1 Ap

Figure 8.1 Current Harmonics

AC Current Waveform


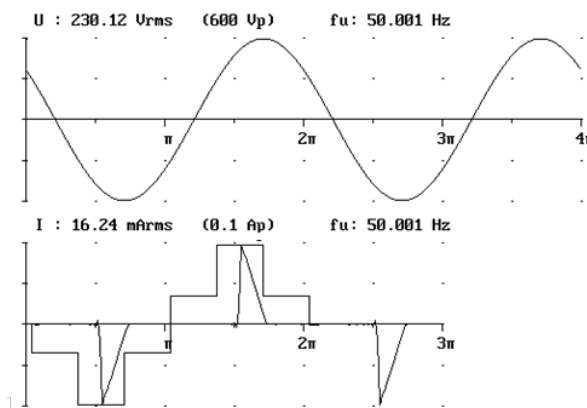



Figure 8.2 AC Current Waveform

8.0 Performance (Cont.)

8.3 Conducted EMI

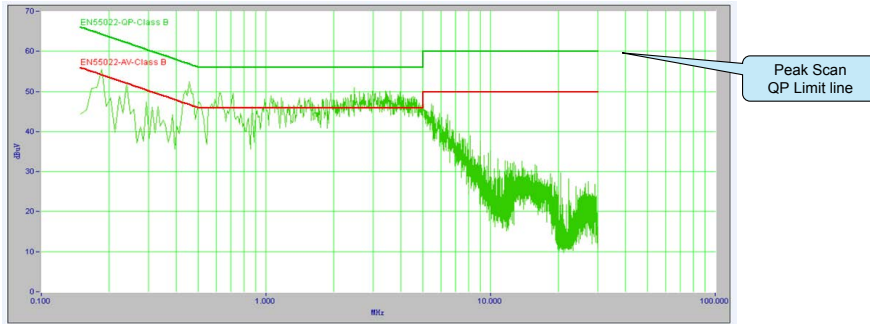

a) Peak Scan L

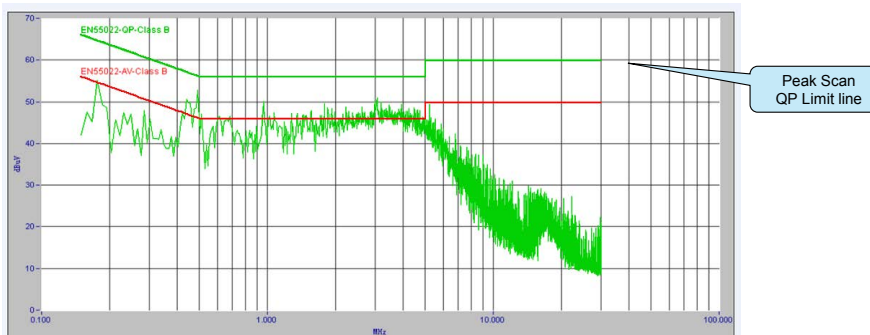

b) Peak Scan N

Figure 8.3 EMI Results



Trademark Information

© 2012 iWatt, Inc. All rights reserved. iWatt, BroadLED, **EZ-EMI**, Flickerless, Intelligent AC-DC and LED Power, and PrimAccurate are trademarks of iWatt, Inc. All other trademarks and registered trademarks are the property of their respective owners.

Contact Information

Web: <http://www.iwatt.com>
E-mail: info@iwatt.com
Phone: +1 (408) 374-4200
Fax: +1 (408) 341-0455

iWatt Inc.

675 Campbell Technology Parkway, Suite 150
Campbell, CA 95008

Disclaimer

iWatt reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. iWatt makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

iWatt cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an iWatt product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage (“Critical Applications”).

IWATT SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of iWatt products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to iWatt, Inc.

iWatt semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

www.iwatt.com

