

Dimmable LED Driver with iW3614
(AC Input 90-135V_{AC}, Output 30V 350mA)

Dimmable LED Driver with iW3614 (AC Input 90-135V_{AC}, Output 30V 350mA) EBC899

1.0. Introduction	3
2.0. Design Features	3
3.0. Design Specification	4
4.0. Schematic	5
5.0. PCB Layout.....	5
6.0. Bill of Materials	6
7.0. Transformer Drawing	7
8.0. Performance	8
8.1. Constant Current and Efficiency	8
8.2. Harmonic and Current Waveform	8
8.3. Conducted EMI	9

1.0 Introduction

This reference design describes a 9 LEDs output at 350mA current, low line input (90–135V_{AC}) power supply for phase-cut dimmable LED applications. For this design the iW3614 is used. This document contains the design features of the phase-cut dimmable LED driver, a detailed circuit diagram, an entire bill of materials required to build the LED driver, a drawing of the power transformer, and test data of the most important performance.

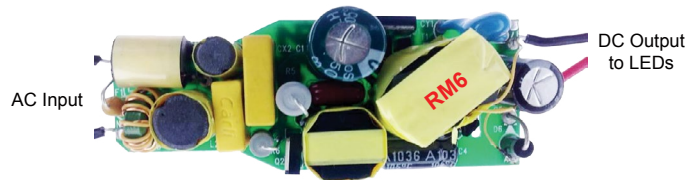


Figure 1.1 PCB Top View

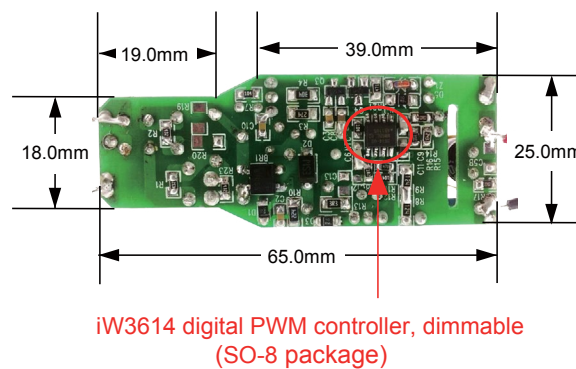


Figure 1.2 PCB Bottom View

2.0 Design Features

- Isolated AC/DC offline, input 120V_{AC}
- Output 9 LEDs at 350mA
- Intelligent wall dimmer detection:
 - » Leading-edge dimmer
 - » Trailing-edge dimmer
 - » No dimmer
- Multiple dimming control schemes
 - » Hybrid dimming
 - » PWM dimming, 900Hz
 - » Amplitude dimming
- Wide dimming range from 1% to 100%
- Flickerless™ LED dimming technology: no visible flicker
- Resonant control to achieve high efficiency
- High power factor, 0.9 without dimmer
- Over-temperature protection and de-rating
- PrimAccurate™ primary-only sensing eliminates opto-isolator feedback and simplifies design

3.0 Design Specification

The table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment
Input						
Voltage	V_{IN}	90		135	V _{AC}	2 wire
Frequency	f_{LINE}	57	60	63	Hz	
Output						
Output voltage	V_{OUT}		30		V	Measured at the end of PCB
Output current	I_{OUT}		0.35		A	
Output ripple current	I_{RIPPLE}		70		mA _{P-P}	Set oscilloscope at 20MHz bandwidth
Total Output Power						
Continuous output power	P_{OUT}		12		W	
Power factor	PF		0.90			Harmonic meet IEC61000-3-2
Efficiency	η		80		%	Measured at end of PCB V _{IN} =115V _{AC} (T _{AMB} =25°C)
Environmental						
Conducted EMI		Meets EN55015B				
Safety		Designed to meet IEC950, UL1950 Class II				
Ambient temperature	T_{AMB}		40		°C	Free convection, sea level

4.0 Schematic



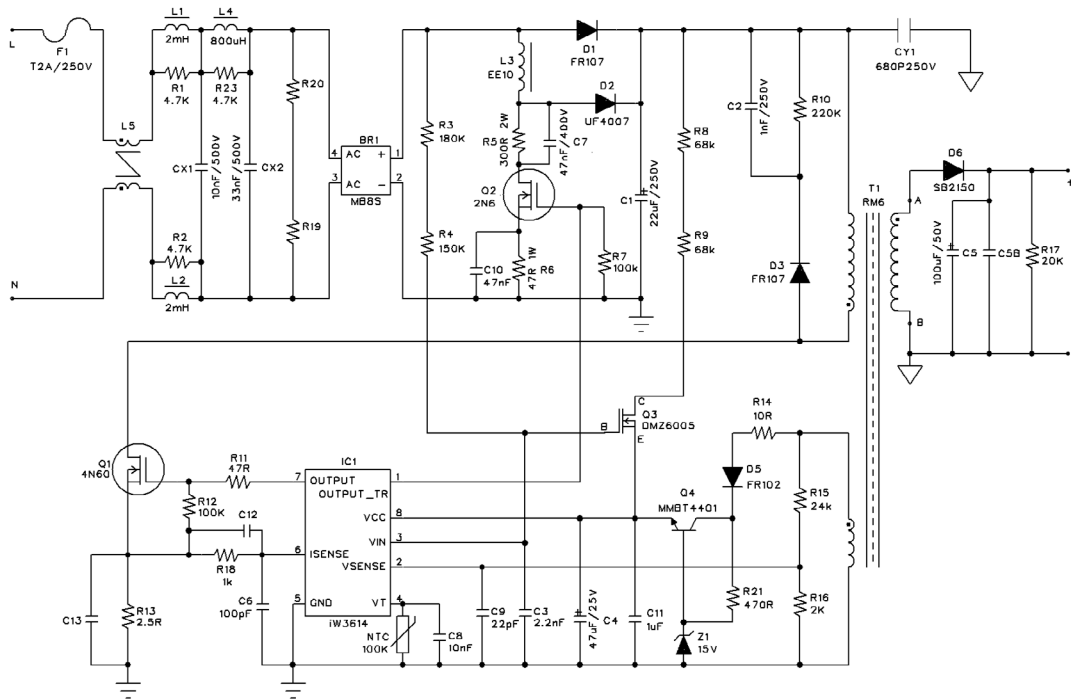


Figure 4.1 Design Schematic

5.0 PCB Layout

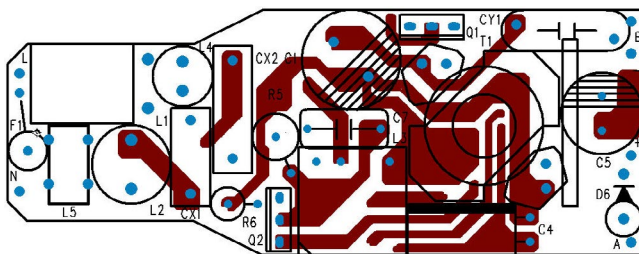

a) PCB Top

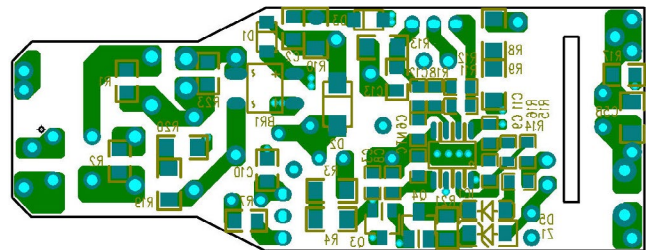

b) PCB Bottom


Figure 5.1 PCB Layout 65.0 mm x 25.0 mm

6.0 Bill of Materials

Item	Qty.	Ref.	Description	Manufacturer P/N	Manufacturer
1	1	IC1	iW3614-00, digital PWM controller, dimmable, SO-8	iW3614-00	iWatt, Inc
2	1	CX1	0.01μF, 275V, X2, Pin=7.5mm	PX103K3IB19H200D9R	CARLI
3	1	CX2	0.033μF, 275V, X2, Pin=10mm	PX333K3IC29H200D9	CARLI
4	1	C7	47nF/400V, CL21, Pin=7.5mm	AF473J2G079L250D9R	CARLI
5	1	C1	22μF, 250V, E-CAP, 105°C	22UFLK250V	Yongming
6	1	C2	1nF, 250V, X7R, SMD 0805	251R15W102KV4E	Johanson
7	1	C3	2.2nF, 50V, X7R, SMD 0805	CL10C222KB8NNNC	Samsung
8	1	C6	100pF, 50V, X7R, SMD 0603	CL10C101KB8NNNC	Samsung
9	1	C8	1nF, 50V, X7R, SMD 0603	CL10C102KB8NNNC	Samsung
10	1	C9	22pF, 50V, X7R, SMD 0603	CL10C220KB8NNNC	Samsung
11	1	C11	1μF, 50V, X7R, SMD 0805	CL10C105KB8NNNC	Samsung
12	1	C10	47nF, 50V, X7R, SMD 0805	CL10C473KB8NNNC	Samsung
13	1	C4	47μF, 25V, E-Cap	47UFLK25V	Yongming
14	1	C5	100μF, 50V, E-Cap	100UFLK50V	Yongming
15	3	R1, R2, R23	4.7kΩ ±5%, SMD-0805	RC0805JR-074K7L	YAGEO
16	1	R3	150kΩ ±1%, SMD-1206	RC1206JR-07150KL	YAGEO
17	1	R4	180kΩ ±1%, SMD-1206	RC1206JR-07180KL	YAGEO
18	1	R5	300Ω ±5%, 2W	300R2W MOF	YAGEO
19	1	R6	47Ω ±5%, 1W	47R1W MOF	YAGEO
20	1	R10	220kΩ ±5%, SMD-1206	RC1206JR-07220KL	YAGEO
21	2	R7, R12	100kΩ ±5%, SMD-0805	RC0805JR-07100KL	YAGEO
22	2	R8, R9	68kΩ ±5%, SMD-1206	RC1206JR-0768KL	YAGEO
23	1	R18	1kΩ ±1%, SMD-0603	RC0603JR-071KL	YAGEO
24	1	R13	2.5Ω ±1%, SMD-1206	RC1206JR-072R5L	YAGEO
25	1	R21	470Ω ±1%, SMD-0805	RC0805JR-07470RL	YAGEO
26	1	R11	47Ω ±5%, SMD-0805	RC0805JR-0747RL	YAGEO
27	1	R14	10Ω ±5%, SMD-0805	RC0805JR-0710RL	YAGEO
28	1	R15	24kΩ ±1%, SMD-0805	RC0805JR-0724KL	YAGEO
29	1	R16	2kΩ ±1%, SMD-0603	RC0603JR-072KL	YAGEO
30	1	NTC	100kΩ ±5%, SMD-0603	RC0603JR-07100KL	YAGEO
31	1	R17	20kΩ ±5%, SMD-0805	RC0805JR-0720KL	YAGEO
32	1	FR1	T2A, 250V	MST2A250V	Conquer
33	1	BR1	DB107S, SMD	KBP1010S	PANJIT
34	2	D1, D3	FR107, 1A1000V, SMD-1206S	SRGC10MH	ZOWEI
35	1	D2	MF4007/ES1J, SMA	ES1J	PANJIT
36	1	D5	FR102, 1A, 1000V, SMD-1206S	SRGC10DH	ZOWEI
37	1	D6	MBR2150, 2A, 150V, DO-41	MBR2150	PANJIT
38	1	Z1	Zener, 15V, LL34	ZVS15V	ST
39	1	CY1	Y1, 680pF, 250V	Y1680PF250V	STF
40	1	Q1	FTU04N60B, 4A, 600V, TO-251	FTU04N60B	ARK
41	1	Q2	FTU2N60B, 2A, 600V, TO-251	FTU02N60B	ARK
42	1	Q3	DMZ6005, N-Depletion, 600V, SOT-23	DMZ6005	ARK
43	1	Q4	MMBT4401, SOT-23	MMBT4401	NXP
44	2	L1, L2	2mH, Drum choke, 8X10mm, 0.21mm, 240Ts	8X10MM	xingyuangyang
45	1	L4	800μH, Drum choke, 6X8mm, 0.17mm, 175Ts	6X8MM	xingyuangyang
46	1	L3	1.2mH, EE10, 0.19mmX240Ts	EE10	xingyuangyang
47	1	L5	25μH, T8X4X3, B29	Common Mode Choke	Bead & Ferrite
48	1	T1	RM6, Transformer	RM6	xingyuangyang

7.0 Transformer Drawing

Schematic:

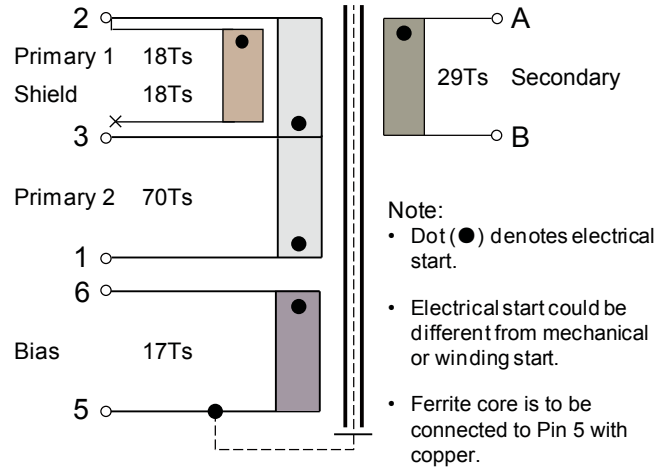

Electrical Specifications:

1. Primary inductance (L_p) = 1.2mH @10kHz
2. Primary leakage inductance (L_k) \leq 50 μ H @10kHz
3. Electrical strength = 3KV, 50/60Hz, 1Min

Materials:

1. Core : RM6 (Ferrite material TDK PC40 or equivalent)
2. Bobbin : RM6, vertical, primary=3, secondary=3
3. Magnet wires (Pri) : type 2-UEW
4. Magnet wire (Sec) : triple insulated wires
5. Layer insulation tape : 3M1298 or equivalent

Finished:

1. Remove pin 4 from the bobbin
2. Core is connected to PRI-GND Pin5
3. Varnish the complete assembly

8.0 Performance

8.1 Constant Current and Efficiency

* Note: V_{IN}=90V_{AC}-135V_{AC}/60Hz; Loading with 9 LEDs 350mA

V _{IN} (V _{AC})	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	Ripple(PK) (mA)	η (%)	Power Factor
90	13.72	29.727	0.359	68	77.81%	0.946
100	13.30	29.698	0.358	64	79.96%	0.945
110	13.06	29.676	0.357	64	81.21%	0.936
115	12.96	29.648	0.357	64	81.67%	0.942
120	12.88	29.63	0.357	64	82.06%	0.937
130	12.76	29.613	0.356	64	82.67%	0.912
135	12.72	29.6	0.356	68	82.91%	0.892

8.2 Harmonic and Current Waveform

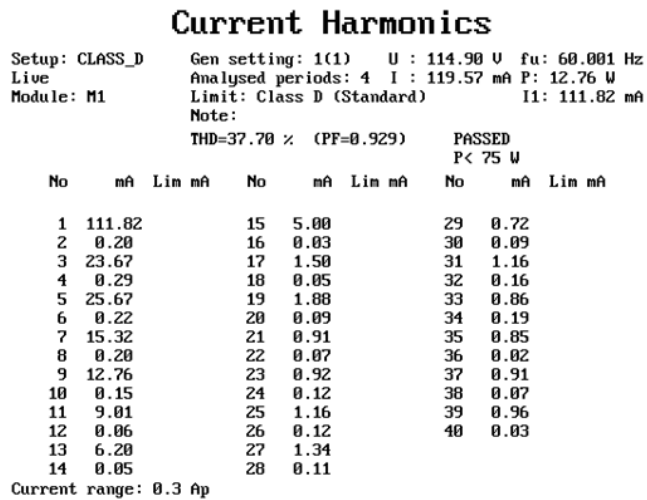


Figure 8.2.1 Current Harmonics @115V_{AC}
Meet IEC61000-3-2 requirement


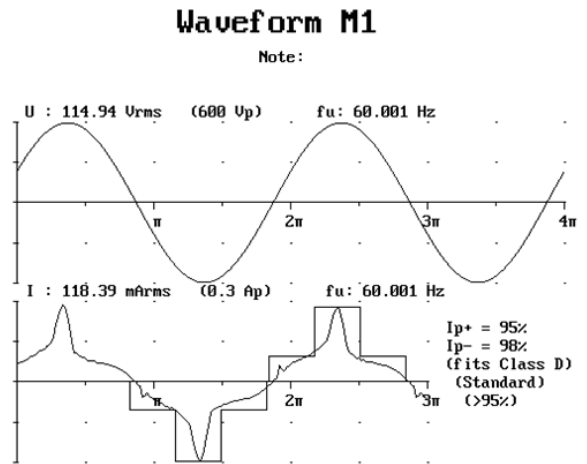



Figure 8.2.2 AC Current Waveform @115V_{AC}
PF=0.929

8.0 Performance (Cont.)

8.3 Conducted EMI

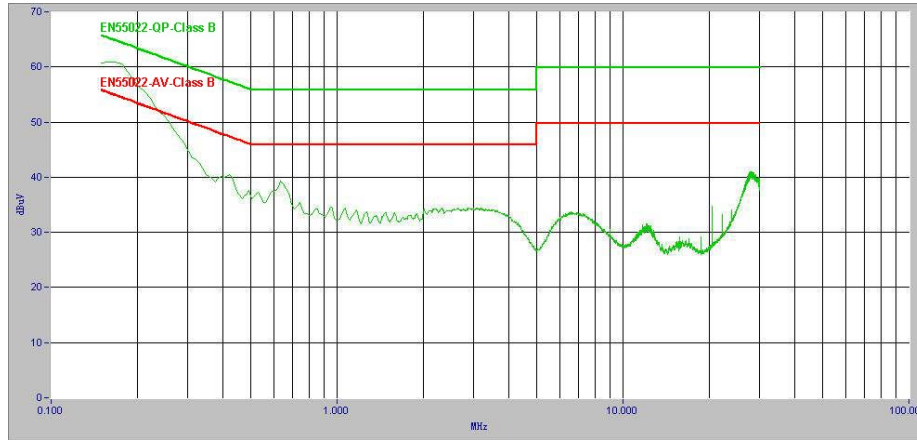

a) QP Scan L

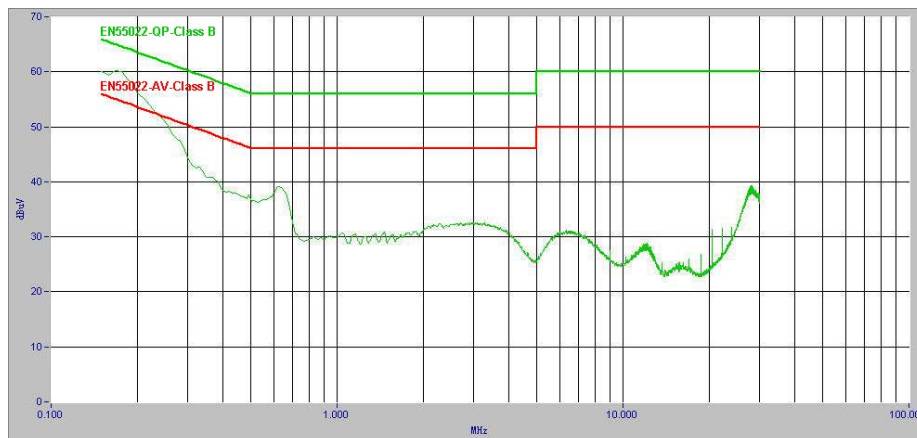

b) QP Scan N

Figure 8.3.1 EMI Results



Trademark Information

© 2013 iWatt Inc. All rights reserved. iWatt, the iWatt logo, and EZ-EMI are registered trademarks and AccuSwitch, BroadLED, Flickerless and PrimAccurate are trademarks of iWatt Inc. All other trademarks and registered trademarks are the property of their respective owners.

Contact Information

Web: <http://www.iwatt.com>

E-mail: info@iwatt.com

Phone: +1 (408) 374-4200

Fax: +1 (408) 341-0455

iWatt Inc.

675 Campbell Technology Parkway, Suite 150
Campbell, CA 95008

Disclaimer

iWatt reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. iWatt makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

iWatt cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an iWatt product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

IWATT SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of iWatt products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to iWatt, Inc.

iWatt semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

www.iwatt.com

