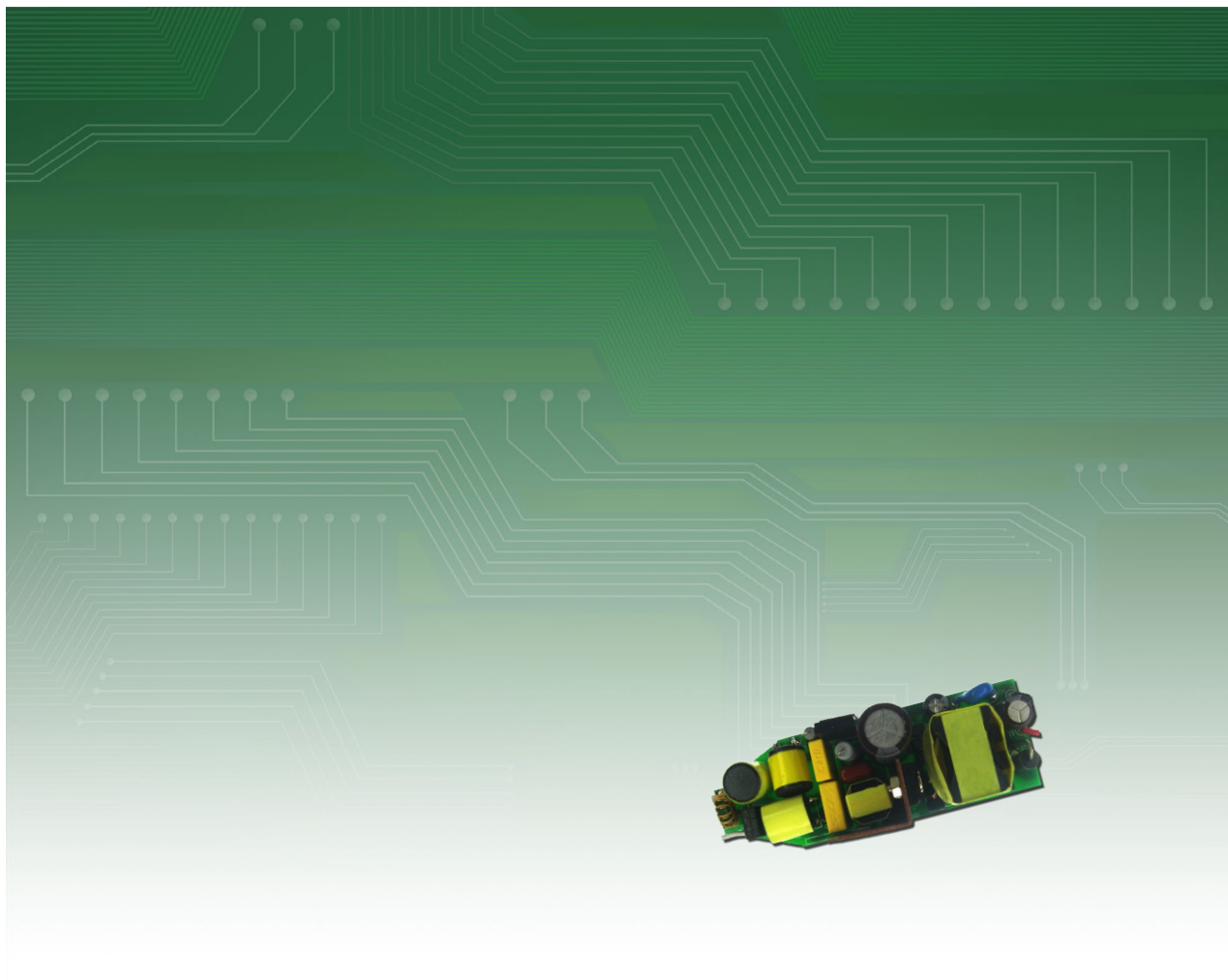




Dimmable LED Driver with iW3614-00

(AC Input 180-264V_{AC}, Output 21V 700mA)

Dimmable LED Driver with iW3614-00

(AC Input 180-264V_{AC}, Output 21V 700mA)

EBC904

1.0. Introduction	3
2.0. Design Features	3
3.0. Design Specification	4
4.0. Schematic	5
5.0. PCB Layout.....	5
6.0. Bill of Materials	6
7.0. Transformer Drawing	8
8.0. Performance	9
8.1. Constant Current and Efficiency	9
8.2. Current Harmonics.....	9
8.3. Conducted EMI	10

1.0 Introduction

This reference design describes a 6 LEDs output, high line input (180–264V_{AC}) power supply for dimmable LED applications. For this design the iW3614-00 is used. This document contains the complete specification of the LED driver, a detailed circuit diagram, an entire bill of materials required to build the LED driver, a drawing of the power transformer, and test data of the most important performance.

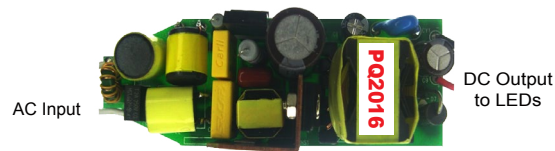


Figure 1.1 PCB Top View

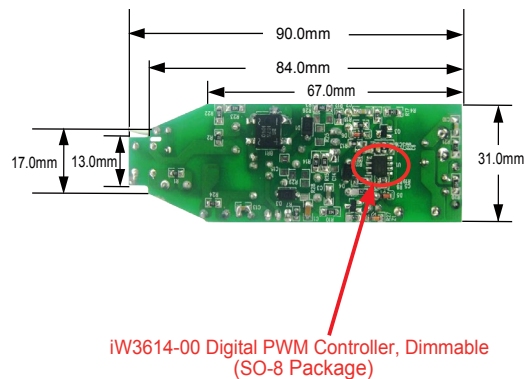


Figure 1.2 PCB Bottom View

2.0 Design Features

- Isolated AC/DC offline, input 230V_{AC}
- Output 6 LEDs at 700mA
- Intelligent wall dimmer detection:
 - » Leading-edge dimmer
 - » Trailing-edge dimmer
 - » No-dimmer
- Multiple dimming control schemes
 - » Hybrid dimming
 - » PWM dimming: 900Hz
 - » Amplitude dimming
- Wide dimming range from 1% to 100%
- Flickerless™ LED dimming technology: no visible flicker
- Resonant control to achieve high efficiency
- High power factor, 0.9-0.98 without dimmer
- Over-temperature protection and de-rating
- PrimAccurate™ primary-only sensing eliminates opto-isolator feedback and simplifies design

3.0 Design Specification

The table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment
Input						
Voltage	V_{IN}	180		264	V _{AC}	2 wire
Frequency	f_{LINE}	47	50	63	Hz	
Output						
Output voltage	V_{OUT}		21		V	Measured at the end of PCB
Output current	I_{OUT}		0.7		A	
Output ripple current	I_{RIPPLE}				mA _{P-P}	Set oscilloscope at 20MHz bandwidth
Total Output Power						
Continuous output power	P_{OUT}		14.7		W	
Power factor	PF	0.9				
Efficiency	η		83		%	Measured at end of PCB $V_{IN}=230V_{AC}$
Environmental						
Conducted EMI		Meets CISPR22B/EN55022B				
Safety		Designed to meet IEC950, UL1950 Class II				
Ambient temperature	T_{AMB}	0		40	°C	Free convection, sea level

4.0 Schematic



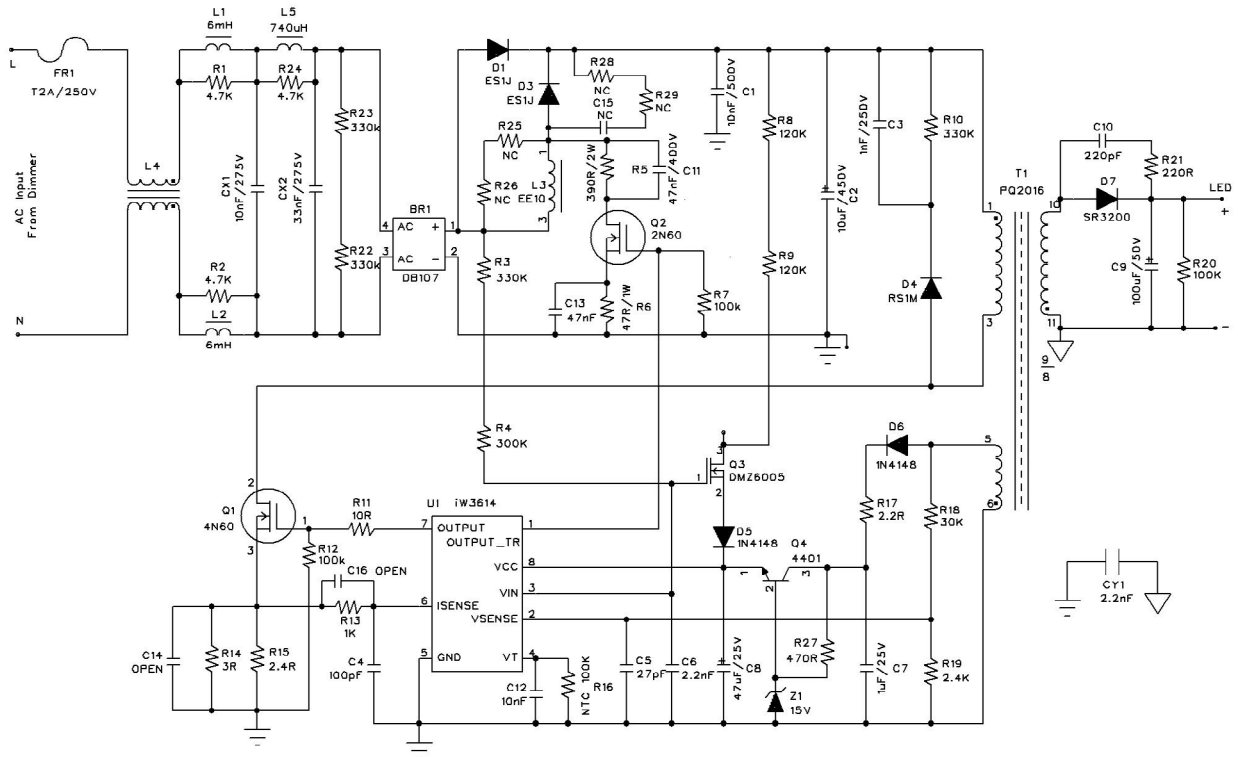


Figure 4.1 Design Schematic

5.0 PCB Layout

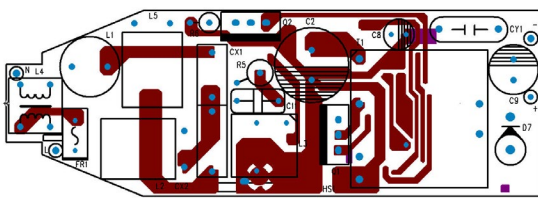

a) PCB Top

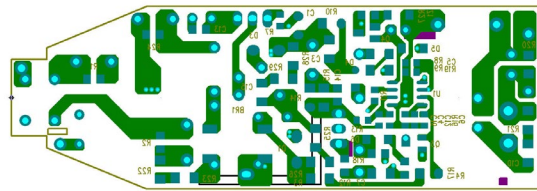

b) PCB Bottom

Figure 5.1 PCB Layout 90mm X 31mm

6.0 Bill of Materials


Item	Qty.	Ref.	Description	Manufacturer P/N	Manufacturer
1	1	U1	iW3614-00, Digital PWM Controller Dimmable, SO-8	iW3614-00	iWatt, Inc.
2	1	CX1	0.01μF, 275V, X2	PX103K3IB19H200D9R	CARLI
3	1	CX2	0.033μF, 275V, X2	PX333K3IC29H200D9R	CARLI
4	1	C11	47nF/400V, CL21 pin=7.5mm	AF473J2G079L250D9R	CARLI
5	1	C2	10μF, 450V, E-cap, 105°C	10μFLK450V	Yongming
6	1	C3	1nF, 250V, X7R, SMD1206	251R15W102KV4E	Johanson
7	1	C4	100pF, 50V, X7R, SMD 0805	CL10C101KB8NNNC	Samsung
8	1	C5	27pF, 50V, X7R, SMD 0805	CL10C27KB8NNNC	Samsung
9	1	C6	2.2nF, 50V, X7R, SMD 0805	CL10C222KB8NNNC	Samsung
10	1	C7	1μF, 50V, X7R, SMD 1206	CL10C105KB8NNNC	Samsung
11	1	C13	47nF, 50V, X7R, SMD 0805	CL10C473KB8NNNC	Samsung
12	1	C10	220pF, 250V, X7R, SMD1206	251R15W221KV4E	Johanson
13	1	C12	10nF, 50V, X7R, SMD 0805	CL10C103KB8NNNC	Samsung
14	1	C8	47μF, 25V, E-cap	47μFLK25V	Samsung
15	1	C9	100μF, 50V, E-cap	100μFLK50V	Samsung
16	3	R1, R2, R24	4.7KΩ, ±5%, SMD-1206	R1206JR-074K7L	Yongming
17	1	R3	330KΩ, ±1%, SMD-1206	RC1206JR-07330KL	Yongming
18	1	R4	300KΩ, ±1%, SMD-1206	RC1206JR-07300KL	YAGEO
19	1	R5	390Ω, ±5%, 2W	390R2W MOF	YAGEO
20	1	R6	47Ω, ±5%, 1W	47R1W MOF	YAGEO
21	1	R10	330KΩ, ±5%, SMD-1206	RC1206JR-07330KL	YAGEO
22	2	R7,R12	100KΩ, ±5%, SMD-0805	RC0805JR-07100KL	YAGEO
23	2	R8,R9	120KΩ, ±5%, SMD-1206	RC1206JR-07120KL	YAGEO
24	1	R13	1KΩ, ±1%, SMD-0603	RC0603JR-071KL	YAGEO
25	1	R14	3Ω, ±1%, SMD-1206	RC1206JR-073RL	YAGEO
26	1	R15	2.4Ω, ±1%, SMD-1206	RC1206JR-072R4L	YAGEO
27	2	R22,R23	330kΩ, ±5%, SMD-1206	RC1206JR-07330KL	YAGEO
28	1	R27	470Ω, ±5%, SMD-0805	RC0805JR-07470RL	YAGEO
29	1	R16	100KΩ, ±5%, SMD-0603 (100K NTC)	RC0603JR-07100KL	YAGEO
30	1	R11	10Ω, ±5%, SMD-0805	RC0805JR-0710RL	YAGEO
31	1	R18	30KΩ, ±1%, SMD-0805	RC0805JR-0730KL	YAGEO
32	1	R19	2.4KΩ, ±1%, SMD-0603	RC0603JR-072K4L	YAGEO
33	1	R20	100KΩ, ±5%, SMD-1206	RC1206JR-07100KL	YAGEO
34	1	R21	220Ω, ±5%, SMD-1206	RC1206JR-07150RL	YAGEO
35	1	F1	T2A250V	MST2A250V	Conquer
36	1	BR1	DB107S, SMD	KBP1010S	PANJIT
37	1	D4	RS1M, SMD	SRGC10MH	ZOWEI
38	2	D3,D1	ES1J, SMD	ES1J	PANJIT
39	2	D5,D6	1N4148 0.1A/100V, SMD	1N4148	PANJIT

6.0 Bill of Materials (Cont.)

Item	Qty.	Ref.	Description	Manufacturer P/N	Manufacturer
40	1	D7	MUR3200 3A/200V D0-201AD	MUR3200	PANJIT
41	1	Z1	Zener, 15V, SMD	ZVS15V	ST
42	1	CY1	Y1, 2.2nF250V	Y12.2NF250V	STF
43	1	Q1	FTA04N60B, TO-220F	FTA04N60B	ARK
44	1	Q2	FTA02N60B, TO-220F	FTA02N60B	ARK
45	1	Q4	MMBT4401, SOT-23	MMBT4401	NXP
46	1	Q3	DMZ6005, N-Depletion, 600V, SOT-23	DMZ6005,	ARK
47	2	L1,L2	6mH, Drum choke, 10X12mm, 0.20mm,400Ts	10X12MM	xingyuangyang
48	1	L5	740μH, Drum choke, 10X12mm, 0.35mm 140Ts	10X12MM	xingyuangyang
49	1	L3	3.6mH, EE10	EE10	xingyuangyang
50	1	L4	Common Mode Inductor T8*4*3 30uH	Common Mode Choke	Bead&Ferrite
51	1	T1	PQ2016, Transformer	PQ2016	xingyuangyang

7.0 Transformer Drawing

Schematic:

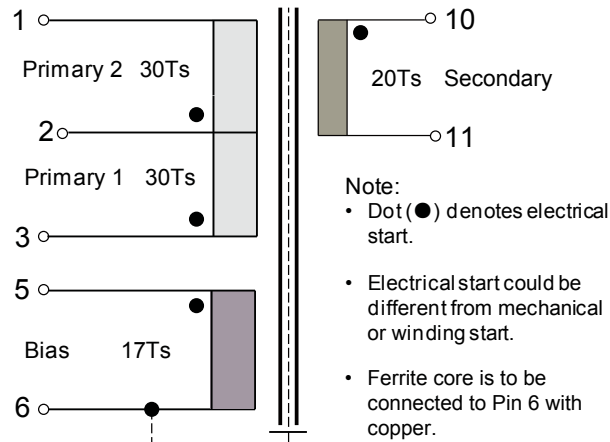

Electrical Specifications:

1. Primary inductance (L_p) = 1.3mH @10KHz
2. Primary leakage inductance (L_k) $\leq 70\mu\text{H}$ @10KHz

Materials:

1. Core: PQ2016 (ferrite material TDK PC40 or equivalent)
2. Bobbin: PQ2016
3. Magnet wires (Pri): type 2-UEW
4. Magnet wire (Sec): triple insulated wires
5. Layer insulation tape: 3M1298 or equivalent

Finished:

1. Remove pins 2, 4, 7, 8, 9, 12, 13, 14 from the bobbin
2. Varnish the complete assembly
3. Core is connected to primary pin 6

8.0 Performance

8.1 Constant Current and Efficiency

* Note: $V_{IN}=180V_{AC}-264V_{AC}/50Hz$; Loading with 6 LEDs 700mA

V_{IN} (V _{AC})	P_{IN} (W)	V_{OUT} (V)	I_{OUT} (mA)	η (%)	Power Factor
180	18.82	22.36	0.705	83.76%	0.954
190	18.69	22.33	0.703	84.03%	0.962
200	18.61	22.31	0.702	84.19%	0.970
210	18.56	22.30	0.702	84.37%	0.974
220	18.50	22.28	0.700	84.35%	0.976
230	18.41	22.26	0.699	84.47%	0.976
240	18.37	22.24	0.698	84.47%	0.972
250	18.36	22.22	0.697	84.35%	0.965
260	18.32	22.21	0.696	84.40%	0.956
264	18.35	22.20	0.696	84.20%	0.952

8.2 Current Harmonics

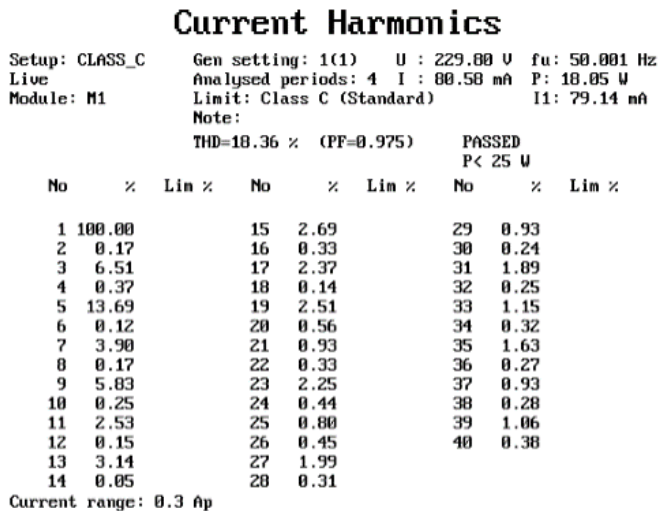


Figure 8.2.1 Current Harmonics


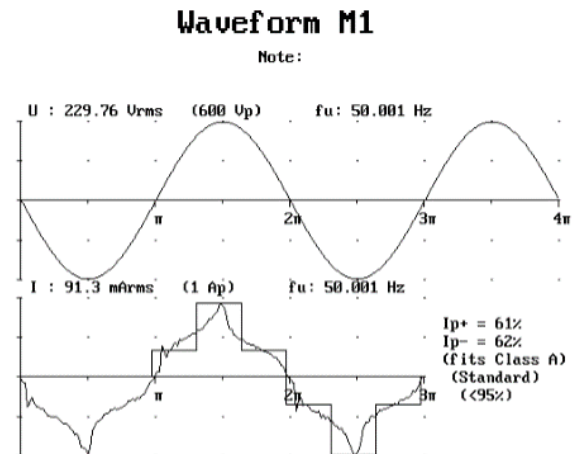



Figure 8.2.2 AC Current Waveform

8.0 Performance (Cont.)

8.3 Conducted EMI

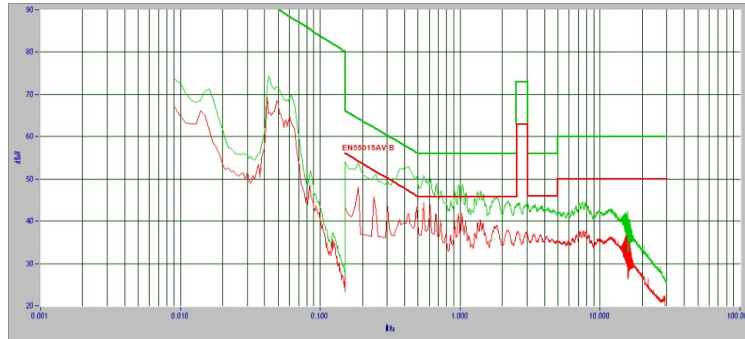

a) QP & AV Scan L

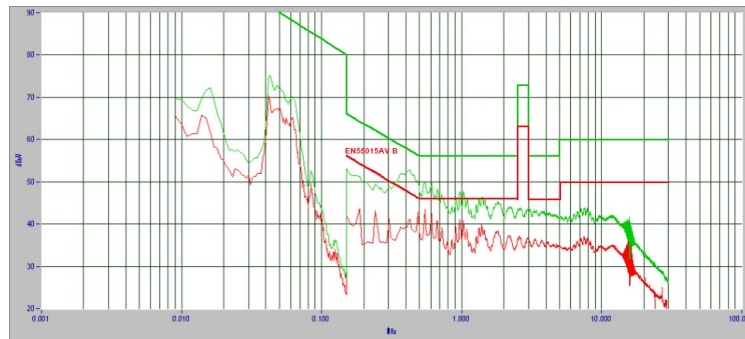

b) QP & AV Scan N

Figure 8.3.1 EMI Results



Trademark Information

© 2013 iWatt Inc. All rights reserved. iWatt, the iWatt logo, and EZ-EMI are registered trademarks and AccuSwitch, BroadLED, Flickerless and PrimAccurate are trademarks of iWatt Inc. All other trademarks and registered trademarks are the property of their respective owners.

Contact Information

Web: <http://www.iwatt.com>

E-mail: info@iwatt.com

Phone: +1 (408) 374-4200

Fax: +1 (408) 341-0455

iWatt Inc.

675 Campbell Technology Parkway, Suite 150
Campbell, CA 95008

Disclaimer

iWatt reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. iWatt makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

iWatt cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an iWatt product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

IWATT SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of iWatt products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to iWatt, Inc.

iWatt semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

www.iwatt.com