

LED Driver with iW3626-00

(AC input 90-264 V_{AC}, Output 100V 80mA)

LED Driver with iW3626-00

(AC input 90-264 V_{AC}, Output 100V 80mA)

EBC932

1.0. Introduction	3
2.0. Design Features	3
3.0. Design Specification	4
4.0. Schematic	5
5.0. PCB Layout.....	5
6.0. Bill of Materials	6
7.0. Transformer Drawing	7
8.0. Performance	8
8.1. Constant Current and Efficiency	8
8.2. Harmonic.....	8
8.3. 8.3 Conducted EMI	9

1.0 Introduction

This reference design describes a 33 LEDs output, universal input (90–264V_{AC}) power supply for non-dimmable LED applications. For this design the iW3626-00 is used. This document contains the complete specification of the LED driver, a detailed circuit diagram, an entire bill of materials required to build the LED driver, a drawing of the power transformer, and test data of the most important performance.

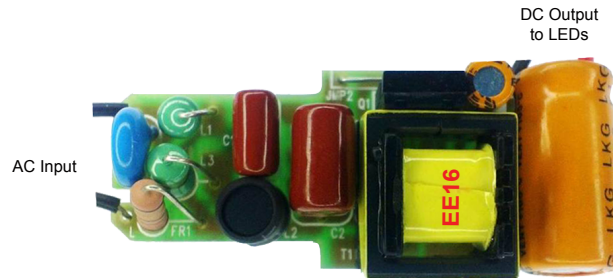


Figure 1.1 PCB Top View

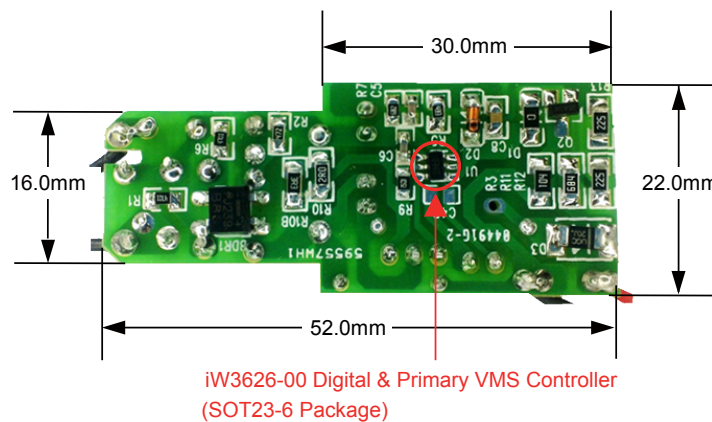


Figure 1.2 PCB Bottom View

2.0 Design Features

- AC input range 90-264V_{AC}
- DC output 100V 80mA(constant current)
- Non-isolated high efficiency
- Single stage high PF with buck boost

3.0 Design Specification

The table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment
Input						
Voltage	V_{IN}	90	230	264	V _{AC}	2 wire
Frequency	f_{LINE}		50		Hz	
Open-load input power (264V _{AC})			150		mW	
Output						
Output voltage	V_{OUT}		100		V	Measured at the PCB connector
Output current	I_{OUT}		0.08		A	
Total Output Power						
Continuous output power	P_{OUT}		8		W	
Over current protection	I_{OUT_MAX}				A	Auto-restart
Power factor	PF	0.7				Harmonic meet IEC61000-3-2
Efficiency	η	88			%	Measured at end of PCB $V_{IN}=100V_{AC}$ ($T_{AMB}=25^{\circ}C$)
Turn on delay time					Sec	
Environmental						
Conducted EMI		Meets EN55015B				
Hi-pot test					KV	
Operation temperature	T_{OPR}		40		°C	Free convection, sea level

4.0 Schematic

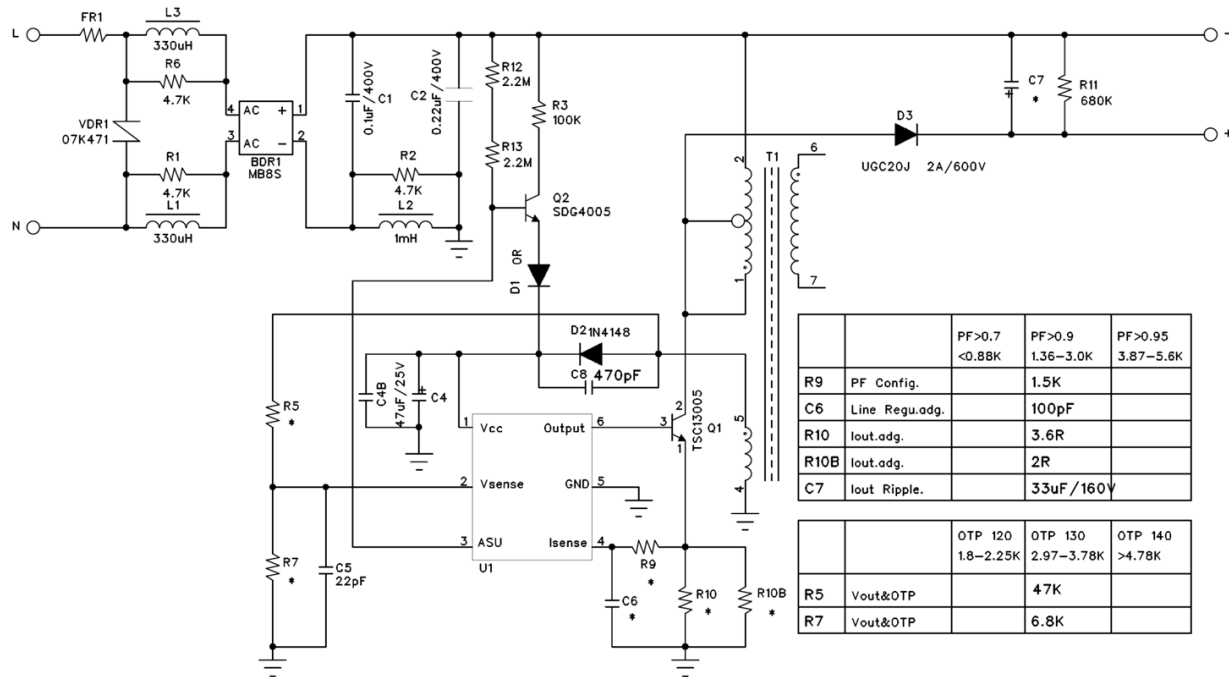


Figure 4.1 Design Schematic

5.0 PCB Layout

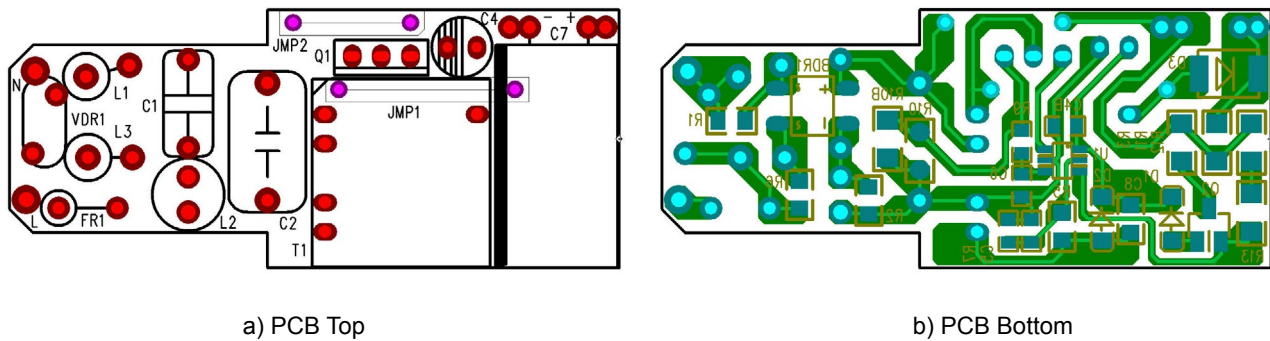



Figure 5.1 PCB Layout 52.0 mm x 22.0 mm

6.0 Bill of Materials

Item	Qty.	Ref.	Description	Manufacturer P/N	Manufacturer
1	1	U1	iW3626-00, off-line digital power controller for LED driver, SOT23-6	iW3626-00	iWatt, Inc
2	1	C1	0.1μF, 400V, CBB, pin=7.5mm	AF104J2G079L250D9R	Carli
3	1	C2	0.22μF, 400V,CBB, pin=10mm	AF224J2G109L250D9R	Carli
4	1	C4	47μF/25V, E-Cap, (Φ5mm×11mm)	47UFLK25V	Yongming
5	1	C7	33μF/160V, E-Cap, (Φ13mm×20mm)	33UFLK200V	Yongming
6	1	C5	22pF/50V, NPO, SMD-0603	CL10C220JB8NNNC	Samsung
7	1	C6	100pF/50V, NPO, SMD-0603	CL10C100JB8NNNC	Samsung
8	1	C8	470pF/50V, X7R, SMD-0805	CL21C471KB8NNNC	Samsung
9	2	L1 ,L2	330μH, 0510	330UF0510	DAXING
10	1	L3	6x8mm, 1.0mH	6X8MM1.0MH	DAXING
11	1	BR1	B8S	B8S	PANJIT Semiconductor
12	1	D1	0Ω, ±5%, SMD-1206	RC1206JR-070RL	YAGEO
13	1	D2	IN4148, LL34	IN4148	PANJIT Semiconductor
14	1	D3	UGC20J, 2A/600V	UGC20J	ZOWEI
15	3	R1,R2,R6	4.7kΩ, ±5%, SMD-0805	RC0805JR-074K7L	YAGEO
16	1	R3	100kΩ, ±5%, SMD-1206	RC1206JR-07100KL	YAGEO
17	1	R5	47kΩ, ±5%, SMD-0805	RC0805JR-0739KL	YAGEO
18	1	R7	6.8kΩ, ±1%, SMD-0603	RC0603FR-075K6L	YAGEO
19	1	R9	1.5kΩ, ±1%, SMD-0603	RC0603FR-074K3L	YAGEO
20	1	R10	2Ω, ±1%, SMD-0805	RC0805FR-071R5L	YAGEO
21	1	R10B	3.6Ω, ±1%, SMD-0805	RC0805FR-075R6L	YAGEO
22	1	R11	680kΩ, ±5%, SMD-0805	RC0805JR-07100KL	YAGEO
23	2	R12 ,R13	2.2MΩ, ±5% SMD-1206	RC1206JR-072M2L	YAGEO
24	1	VDR1	VDR, 07D471	TVR07471KSY	Thingking Electronic
25	1	FR1	10Ω, 1W fusible resistor wirewound resistor	KNP1WST-52-J-10R	ShunChi Electronic
26	1	Q2	3DG4005	33DG40005AS-H	Huajing
27	1	JMP1	15mm, 0.5mm		
28	1	JMP2	10mm, 0.5mm		
29	1	Q1	BTR13005GD, TO-126	BTR13005GD	IPS
30	3	"L,N,+"	UL3239/24AWG, L=60mm, striped and tin plated 3mm, red color		
31	1	"-"	UL3239/24AWG, L=60mm, striped and tin plated 3mm, black color		
32	1	PCB	FR-4, single sided board, 60*23*1.5mm,1oZ		
33	1	Transformer	EE-16 horizontal type		Xingyuanyang

7.0 Transformer Drawing

Schematic:

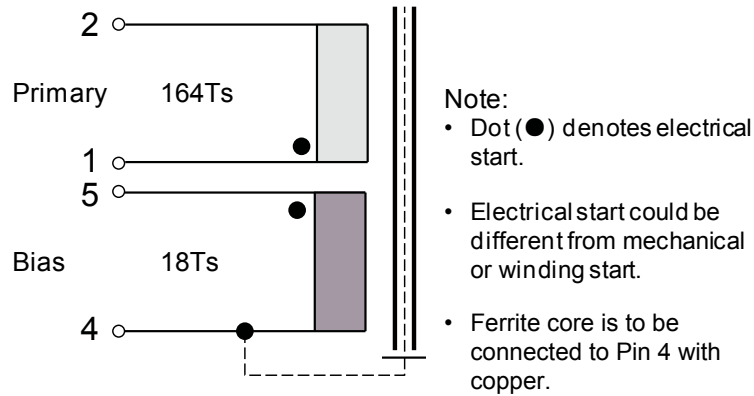

Electrical Specifications:

1. Primary Inductance (L_p) = 1.5mH @10KHz
2. Primary Leakage Inductance (L_k) ≤ 150uH@10KHz

Materials:

1. Core : EE16 (Ferrite Material TDK PC40 or equivalent)
2. Bobbin : EE16
3. Magnet Wires : Type 2-UEW
4. Layer Insulation Tape : 3M1298 or equivalent.

Finished:

1. Varnish the complete assembly
2. Core is connected to pin4(primary ground)

8.0 Performance

8.1 Constant Current and Efficiency

* Note: AC input 90-264V_{AC}, Output 33 LEDs, PF configuration R=1.3KΩ/C=100pF

V _{IN} (V _{AC})	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (mA)	Ripple(PK) (mA)	η (%)	Power Factor
90	8.830	98.16	80.0	91	88.93%	0.94
100	8.770	97.96	80.1	91	89.47%	0.94
110	8.730	97.9	80.3	90	90.05%	0.93
120	8.710	97.85	80.6	90	90.55%	0.93
135	8.800	97.92	81.9	90	91.13%	0.91
150	8.920	97.98	83.2	90	91.39%	0.89
160	8.910	97.98	83.4	90	91.71%	0.88
170	8.880	97.96	83.4	88	92.00%	0.87
180	8.820	97.92	83.0	88	92.15%	0.87
190	8.730	97.87	82.3	87	92.26%	0.87
200	8.630	97.82	81.4	87	92.27%	0.86
210	8.630	97.84	81.4	86	92.28%	0.84
220	8.610	97.83	81.2	86	92.26%	0.83
230	8.590	97.82	81.0	86	92.24%	0.82
240	8.550	97.8	80.8	86	92.42%	0.8
250	8.540	97.8	80.6	86	92.30%	0.79
264	8.510	97.78	80.3	86	92.26%	0.77

8.2 Harmonic

Current Harmonics

Setup: CLASS_C
Live
Module: M1

Gen setting: 1(1) U : 119.73 V fu: 60.001 Hz
Analysed periods: 4 I : 82.53 mA P: 9.24 W
Limit: Class C (Standard) I1: 78.21 mA
Note:
THD=33.65 % (PF=0.935) PASSED
P < 25 W

No	mA	Lin	mA	No	mA	Lin	mA	No	mA	Lin	mA
1	78.21			15	0.72			29	0.87		
2	0.02			16	0.05			30	0.01		
3	25.82			17	1.12			31	0.57		
4	0.00			18	0.02			32	0.02		
5	0.81			19	1.00			33	0.55		
6	0.00			20	0.03			34	0.03		
7	3.58			21	0.57			35	0.50		
8	0.00			22	0.05			36	0.04		
9	0.80			23	0.43			37	0.50		
10	0.02			24	0.04			38	0.02		
11	1.71			25	0.75			39	0.71		
12	0.04			26	0.02			40	0.02		
13	1.20			27	1.02						
14	0.04			28	0.03						

Current range: 0.3 A

Figure 8.2.1 Current Harmonics, PF>0.9, V_{IN}=110V_{AC}

Current Harmonics

Setup: CLASS_C
Live
Module: M1

Gen setting: 1(1) U : 229.71 V fu: 60.001 Hz
Analysed periods: 4 I : 49.39 mA P: 9.19 W
Limit: Class C (Standard) I1: 46.11 mA
Note:
THD=38.08 % (PF=0.810) PASSED
P < 25 W


No	mA	Lin	mA	No	mA	Lin	mA	No	mA	Lin	mA
1	46.11			15	1.55			29	1.09		
2	0.02			16	0.02			30	0.05		
3	15.43			17	1.43			31	0.89		
4	0.01			18	0.02			32	0.03		
5	4.65			19	1.08			33	0.75		
6	0.02			20	0.01			34	0.07		
7	3.66			21	1.01			35	0.81		
8	0.01			22	0.04			36	0.01		
9	3.05			23	0.98			37	0.73		
10	0.00			24	0.03			38	0.03		
11	2.77			25	1.01			39	0.69		
12	0.04			26	0.03			40	0.05		
13	2.08			27	1.10						
14	0.02			28	0.04						

Current range: 0.1 A


Figure 8.2.2 Current Harmonics, PF>0.9, V_{IN}=230V_{AC}

8.0 Performance (Cont.)

8.3 Conducted EMI

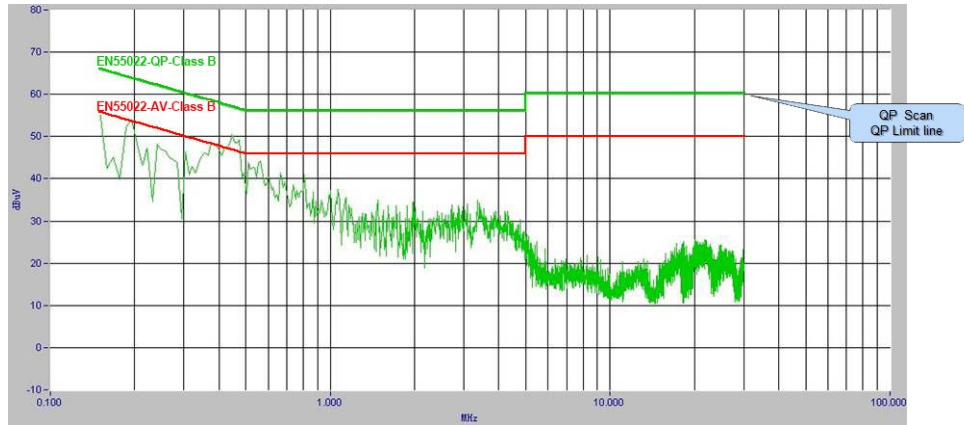

a) QP Scan L

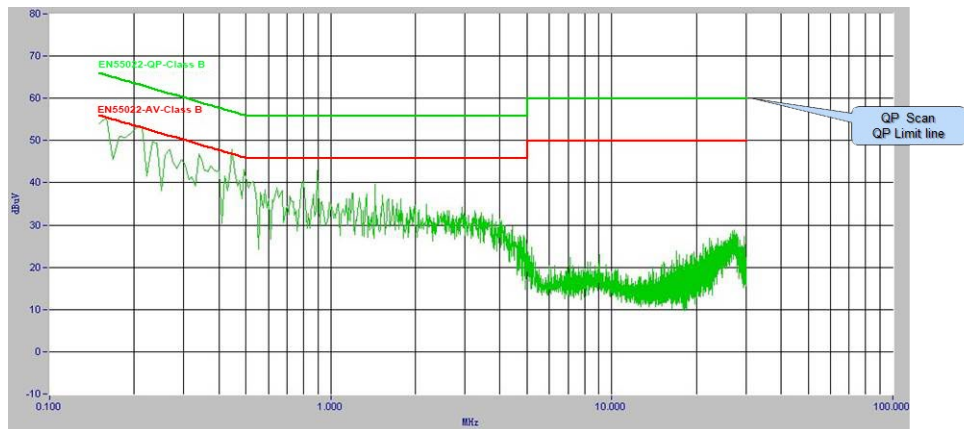

b) QP Scan N

Figure 8.3 EMI Results



Trademark Information

© 2013 iWatt Inc. All rights reserved. iWatt, the iWatt logo, and EZ-EMI are registered trademarks and AccuSwitch, BroadLED, Flickerless and PrimAccurate are trademarks of iWatt Inc. All other trademarks and registered trademarks are the property of their respective owners.

Contact Information

Web: <http://www.iwatt.com>

E-mail: info@iwatt.com

Phone: +1 (408) 374-4200

Fax: +1 (408) 341-0455

iWatt Inc.

675 Campbell Technology Parkway, Suite 150
Campbell, CA 95008

Disclaimer

iWatt reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. iWatt makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

iWatt cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an iWatt product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

IWATT SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of iWatt products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to iWatt, Inc.

iWatt semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

www.iwatt.com

