

μ PC1477C

FM DEMODULATOR FOR DBS RECEIVER

SILICON BIPOLAR MONOLITHIC INTEGRATED CIRCUIT

DESCRIPTION


μ PC1477C is designed for PLL demodulator in DBS receivers(Indoor Unit). μ PC1477C have the functions of phase detector, DC amplifier, and VCO with buffer amplifier.

μ PC1477C is able to operate as high as 600MHz for 2nd IF of DBS receiver by incorporating high f_T transistors into the circuit, and it is obtained wide PLL capture range with external variable capacitance diode.


FEATURES

- Low differential gain and low differential phase(2%, 2° typ.)
- High S/N ratio(60dB typ.)
- Wide PLL capture range(+20MHz typ. @ $f_0=400\text{MHz}$)

PACKAGE DIMENSIONS(Unit:mm)

 

BLOCK DIAGRAM

 

NEC cannot assume any responsibility for any circuits shown or represent that they are free from patent infringement.
NEC reserves the right to make changes at any time without notice in order to improve design and supply the best product possible.

NEC Corporation

www.DataSheet4U.com

APPLICATION OF THE uPC1477C

DESIGN OF FM DEMODULATOR FOR THE DBS RECEIVER

1. INTRODUCTION

The uPC1477C is a monolithic integrated circuit designed for demodulation of high-frequency, wide-band FM signals.

It is the most suitable for the FM demodulator in the DBS receiver.

There are three factors that must be given special consideration when designing the FM demodulator for the DBS receiver:

- Low C/N (approaching the threshold level of the FM demodulator).
- Wide frequency deviation
- Few 2nd IF frequencies to choose from

Although there are various FM demodulating method, the following are most commonly used:

- Dual synchronization
- Delayed detection
- PLL detection

Each of these method can be used for FM demodulation of wide frequency deviation signal. The PLL detection method in particular provides a filter to limit the noise band in the loop, and has good demodulation characteristics at low C/N. It is also suitable for use in an IC. Therefore, the uPC1477C utilizes PLL detection.

2. DESCRIPTION OF THE uPC1477C

The uPC1477C have multiplier which is designed by using dual differential amplifiers for the phase detector.

The VCO is colpitts type oscillator which is used external varicap diode in order to cover wide deviation.

The VCO output signal is injected into the phase detector with $\pm 180^\circ$ phase difference by the buffer amplifier for the VCO.

The uPC1477C also contains DC amplifier in order to get enough loop gain.

3. SELECTING THE 2ND IF FREQUENCY

If we look at the 2nd IF frequencies used in Japan for the DBS receiver, we find that there are just two, 130MHz and 400MHz. However, in the rest of the world, various other frequencies are also used, including 70MHz, 480MHz, 612MHz.

Selection of the best 2nd IF frequency depends primarily on image rejection and the characteristics of the filter to be used in the 2nd IF stage. However, this 2nd IF frequency will have influence on the characteristics of the FM demodulator.

For example, the primary consideration when using the uPC1477C is selection of an appropriate varicap diode for the VCO. If the same item is used at 130MHz and 400MHz, the feed back voltage will be much larger in order to cover regulate FM deviation at 130MHz application. Therefore, the non-linearity of varicap diode will adversely influence various characteristics after demodulation. The following products are recommended for use with each 2nd IF frequency:

* 130MHz : 1SV184

www.DataSheet4U.com

* over 400MHz : 1S2208(B)

The characteristics of the uPC1477C as described in this application note based on use of a 400MHz 2nd IF frequency.

4. LPF DESIGN

In designing a PLL demodulator, the most important point is design of the LPF. Generally, there are three kind of LPF (lag, lag/lead, active filter). Here, we will use a lag/lead filter.

 


Figure 1 Lag/Lead Filter

The transfer function for the lag/lead filter shown in Figure 1 can be given as :

$$H(s) = \frac{W_n^2 + W_n \left(2\zeta - \frac{W_n}{K_\phi K_V K_D} \right) s}{s^2 + 2\zeta W_n s + W_n^2}$$

Where

K_ϕ : Phase detector gain

K_V : VCO gain

K_D : DC Amp gain

W_n : Natural loop frequency

ζ : Loop damping factor

$$W_n = \sqrt{\frac{K_\phi K_V K_D}{T_1 + T_2}} \quad \dots \dots \dots \textcircled{1}$$

$$\zeta = \frac{W_n}{2} \left(T_2 + \frac{1}{K_\phi K_V K_D} \right) \quad \dots \dots \dots \textcircled{2}$$

4.1 W_n

The W_n can be determined by the relation $W_n = W_n t/t$ in Fig.2 which described as PLL indicial response. In this case, the optional lock-up time is necessary to determine initially. However, when using a PLL for the demodulator, it is also necessary to limit the loop noise band. Thus, W_n must be initialized.

In Japan, it is recommended that the 2nd IF in the DBS receiver have a bandwidth of 27MHz at -3dB.

Therefore, this value can be used as W_n ($=2\pi f$).

Care must be exercised in setting the value of W_n . If a small W_n is chosen to make the noise band narrower, this will also attenuate the signal around the maximum frequency deviation and decrease C/N.

This could easily generate truncation noise.

On the other hand, if a large W_n is chosen to increase the capture range, the noise band will be made wider, therefore, degrade S/N after demodulation. In general, W_n should be set to twice the maximum modulation frequency + Δf (the frequency deviation). Thus, for a video signal, W_n should be $17\text{MHz}_{\text{p-p}} + 4.5\text{MHz} \times 2 = 26\text{MHz}$.



Therefore, the 27MHz 2nd IF bandwidth value quoted above is a proper value, and gives the W_n as follows.

$$\begin{aligned} W_n &= 2 \times 27 \times 10^6 \\ &= 1.7 \times 10^8 \end{aligned}$$

  4.2 ζ (DAMPING FACTOR)

It is also necessary to determine the initial damping factor.

Figures 2 and 3 show the indicial response and the closed-loop frequency characteristics for a lag/lead filter applied to a PLL circuit, respectively.



According to Figures 2 and 3, the ζ should be chosen large value in order to get stable loop, but it decreases the amount of attenuation at the out of the band ($\frac{W}{W_n} > 1$), and increases noise in the loop. The figures also show that reducing ζ is a good way to increase attenuation of the signal at the out of the band, however, W_{nt} will be large until the loop stabilizes, so overshoot will be larger.

A ζ of 0.707 is often used (however any ζ of more than 0.3 will cause no trouble).

4.3 PHASE DETECTOR GAIN

The gain of the phase detector in the uPC1477C can be determined as follows.

$$K_\phi = \alpha \cdot V_{in} \cdot A_\phi \cdot \frac{2}{\pi} \text{ (V/rad)} \quad \dots \dots \dots \quad (3)$$

$$\alpha = \frac{h_{fe}}{1 + h_{fe}} = \frac{4}{1 + 4} = 0.8 \quad ; f_T \text{ of a transistor in the uPC1477C is } 1.5 \text{GHz. When an operating frequency of } 0.4 \text{GHz is applied, } \therefore h_{fe} = 4$$

V_{in} : The input voltage is set by AGC Amplifier. This voltage is normally 200mVp-p (-10dBm).

A_ϕ : The gain of the phase detector can be found from the $R_L/r_e + R_E$ for the circuit.

From Figure 4

$$r_e = \frac{26 \text{ mV}}{3.8 \text{ mA}} = 6.8 \Omega$$

$$R_E = 240/3 = 80 \Omega$$

$$R_L = 180 \Omega$$

$$\therefore A_\phi = \frac{180}{6.8 + 80} = 2.07$$

From equation ③

$$K_\phi = 0.8 \times 0.2 \times 2.08 \times 2/\pi$$

$$= 0.211 \text{ V/rad}$$

 


Figure 4 Phase detector


Equivalent Circuit

4.4 VCO GAIN

The gain for the VCO is calculated from the following equation

$$K_V = \frac{\Delta f}{\Delta V} \cdot 2\pi (\text{rad/v.s})$$

 As shown in Figure 5, the VCO frequency change is 10MHz per volt.



4.5 DC AMP. GAIN

As shown in Figure 6, the DC Amp. gain is 27dB (22.4 times).

 


Figure 6 DC Amp Gain vs. Frequency

4.6 DETERMINING THE LPF CONSTANT VALUES

First, T_2 must be determined from Equation ②:

$$\zeta = \frac{W_s}{2} \left(T_2 + \frac{1}{K_\phi K_V K_D} \right)$$

Next, we insert the value of T_2 into Equation ① to

determine T_1 .

$$W_n = \sqrt{\frac{K_d K_v K_D}{T_1 + T_2}}$$

$$= \frac{0.211 \times 6.28 \times 10^7 \times 22.4}{(1.7 \times 10^8)^2} - 4.95 \times 10^{-9}$$

$$= 5.32 \times 10^{-9}$$

Then, we determine the value of C or R_2 using Equation ④,

$T_2 = R_2 C$. If $C = 100\text{pF}$, then

$$R_2 = \frac{4.95 \times 10^{-9}}{100 \times 10^{-12}} = 49.5 (\div 50 \Omega)$$

From Equation ⑤,

$$R_1 = \frac{5.32 \times 10^{-9}}{100 \times 10^{-12}} = 53.2 (\div 50 \Omega)$$

Thus, from the above calculations, the components in the lag/lead filter shown in Figure 1 have the following constant values:

 


Figure 7 Lag/Lead Filter Values

The LPF is applied at two places to the uPC1477C:
between terminals 4 and 2, and between terminals 5 and 1.
The series resistor, R_1 , is also used as the bias resistor for
the DC Amp.

5. INPUT LEVEL TO THE uPC1477C

The data shown in Figure 8 correlates uPC1477C input level to capture and lock ranges. The capture range should be higher than the 27MHz 2nd IF bandwidth. As show in the figure, Pin $\geq -13\text{dBm}$ achieves this requirement.

 


Figure 8 Capture/Lock Range vs. Input power

One method of determining the best input level is to look at the triangular noise after demodulation. This triangular noise is a particular FM noise which increases at a high-frequency area, therefore the S/N will degrade at a high-frequency area of the video signal.

It is called triangular noise because it takes the shape shown in Figure 9.

This type of noise is usually prevented by the use of pre-emphasis (strengthening of the high-frequency ingredients in the video signal before modulating the carrier) during transmission, and the high-frequency of the demodulated video signal is reduced by the de-emphasis.

 


Figure 9 Noise spectrum

 


Figure 10 Effect of Pre-emphasis on Triangular Noise

The triangular noise spectrum is determined by input signal level to the demodulator. It is the most suitable input signal level when the ideal triangular noise spectrum is observed.


The output triangular noise spectrum for various input levels to the uPCL477C are shown in picture 1.

These pictures are observed at the white noise on the unmodulated carrier.


From the viewpoint of capture or lock range, an input level at least -13dBm is sufficient but, as shown by the pictures, if the input level is more than 0dB, the increase in triangular noise at the high end of the band becomes excessive.

Because, the uPCL477C is not included a limitter in front of the phase detector. Thus, the gain of the loop is increased to get the output voltage proportional to the input level, if the input level is set too high, it will generate to parasitic oscillation of the loop.

 
It has been found that the best input level for the uPCL477C uPCL477C is between -7 and -10dBm.



(a) $P_{in} = +5 \text{ dBm}$

 

(b) $P_{in} = -7 \text{ dBm}$

 

(c) $P_{in} = -13 \text{ dBm}$

Picture 1 Triangular Noise Spectrum

6.. THRESHOLD LEVEL

The carrier is transmitted through space which is approximately 36,000km away from the satellite.

This distance greatly attenuates the carrier and decreases C/N. Even though a C/N of 14dB could be ensured in an ordinary receiving, C/N could still be degraded by various unexpected conditions between the satellite and receiver.

Therefore, the FM demodulator requires a type of threshold extention. Usually, this threshold extention is described as the C/N value at that point on the S/N (after demodulation) vs. C/N curve where the S/N is 1dB degraded than the change in C/N.

To confirm the threshold level for the uPC1477C, set up the measurement system show in Figure11. The data for S/N vs. C/N should be as shown in Figures 12 and 13.

 


Figure 11 Block-Diagram for C/N, S/N Measurement

Figure 11 shows block-diagram for C/N, S/N measurement. The FM modulator output signal is made 17MHz modulation by white signal. Generate the white noise on a sparate line containing an attenuator that can be used to vary the white noise level. Make a composite of these signals and supply them through a 27MHz BPF to the $\mu\text{PC1477C}$. Measure the S/N ratio after demodulation using a video noise meter. The LPF in this meter should be set to 4.2MHz.

Figure 12 shows the demodulated S/N curve which is changed C/N values at wide range.

N E C ELECTRONICS INC 98 DE 6427525 0018141 7 T-77-09
As shown in Figure 12, S/N saturates at about 60dB when the
C/N is increased exceedingly.

The data shown in Figure 13 which is confirmed the threshold level.

According to Figure 13, the threshold C/N level is 7dB, so the uPC1477c is extended 3dB than conventional FM demodulator which has the threshold C/N level of 10dB.

 


Figure 12 C/N vs. S/N


 


Figure 13 C/N vs. S/N

 7. TYPICAL APPLICATION CIRCUIT AND ELECTRICAL CHARACTERISTICS

N E C ELECTRONICS INC 98 DE 6427525 0018142 9 D T-77-09



L_1 ; 2 Turns , Core Diameter 5mm

Wire Diameter 1mm

L_2 ; TOKO YTKENBS-28905NY

T_1 ; TDK WBT5.5P5-C10129A

Figure 14 Typical Application Circuit



Figure 15 Printed Board for Typical Application Circuit

Table 1 uPC1477C Electrical Characteristics

Item	Symbol	MIN.	TYP.	MAX.	Unit	Conditions
Circuit Current	I _{cc}	55	65	75	mA	with no signal applied
Capture Range		±15	±20		MHz	$f_0 = 400 \text{ MHz}, P_{in} = -10 \text{ dBm}$
Lock Range		±20	±25		MHz	
Differential Gain	DG		2.0	3.5	%	$P_{in} = -10 \text{ dBm}, f_0 = 400 \text{ MHz}$ $\Delta f_m = 17 \text{ MHz}, \text{--}, \text{Stair Signal}$
Differential Phase	DP		2.0	3.5	deg	
Video S/N	S/N	55	60		dB	$f_0 = 400 \text{ MHz}, P_{in} = -10 \text{ dBm}, \text{White Signal}$
VCO Sensitivity		8	10		MHz/V	$f_0 = 400 \text{ MHz}$
VCO Drift	Δf_{osc}		±1.0	±2.0	MHz	$f_0 = 400 \text{ MHz}, 12 \text{ V} \pm 10 \%$

Figure 14 shows a typical application circuit for the uPC1477C and the printed board shown in Figure 15. Electrical characteristics of the uPC1477C are shown in Table 1.

Although not shown in application circuit, de-emphasis must be inserted after demodulation. In this case, the de-emphasis circuit should be inserted to output terminal (16pin), and should be connected to the next stage through an emitter follower circuit.

525 N E C ELECTRONICS INC

98D 18144

D

T-77-0%

A typical de-emphasis circuit is shown in Figure 16 for reference.

 


Figure 16 Typical De-emphasis Circuit

The characteristics of the application circuit are listed in Table 1.

All characteristics obtained here meet actual requirements for the DBS receiver. Especially DG, DP values are excellent such as 2%, 2° respectively.

Test results at 400MHz are introduced above.

In addition frequency response of the uPC1477C is quite good so it operates both at 130MHz and 612MHz with slight modification of circuits.

Absolute Maximum Ratings ($T_a = 25^\circ\text{C}$)

Supply Voltage	V _{CC}	14.5	V
Power Dissipation	P _T ($T_a = 75^\circ\text{C}$)	910	mW
Operating Temperature	Top:	-20 to +75	°C
Storage Temperature	T _{stg}	-40 to +125	°C

RECOMMENDED OPERATING CONDITIONS

CHARACTERISTIC	SYMBOL	MIN.	TYP.	MAX.	UNIT	UNIT
Supply Voltage	V _{CC}	10.8	12.0	13.2	V	
Input Level	Pin	-13		-5		dBm

ELECTRICAL CHARACTERISTICS ($T_a = 25^\circ\text{C}$, V_{CC} = 12V)

CHARACTERISTICS	SYMBOL	MIN.	TYP.	MAX.	UNIT	TEST CONDITIONS
Total Supply Current	I _{CC}	55	65	75	mA	Zero Carrier
PLL Capture Range		±15	±20		MHz	f ₀ = 400MHz, Pin = -10dBm
PLL Lock Range		±20	±25		MHz	"
Differential Gain	DG		2.0	3.5	%	f ₀ = 400MHz, Pin = -10dBm
Differential Phase	DP		2.0	3.5	deg	f ₀ = 17MHz, Stair Step
Signal to Noise Ratio	S/N	55	60		dB	f ₀ = 400MHz, Pin = -10dBm
VCO Sensitivity		8	10		MHz/V	f ₀ = 17MHz, White Signal
VCO Freq. Drift		±1.0	±2.0		MHz	f ₀ = 400MHz, V _{CC} + 10%