

### KEY FEATURES AND ADVANTAGES

- Advanced primary sensing control circuitry achieves accurate voltage and current (CV and CC) regulation
- Bipolar junction transistor (BJT) primary switch enables ultra low BOM cost design solutions
- Fast start-up performance without additional active components for low BOM cost
- Adaptive base and emitter switching extends RBSOA
- Less than 30 mW no-load power with less than one second turn-on delay and class leading load-transient performance
- Output transient detection (TD) function for very low no-load power applications
- Optimised PWM/PFM with quasi resonant switching enables efficiency standards compliance with margin
- Frequency dithering algorithm allows EMI compliance with margin
- Enables fully compliant solutions for “MoU” universal USB chargers
  - Optimised control of the primary switch drive for low EMI and compliance to EN 301 489-34
  - Inherently low ripple and low EMI enable compliance with the interoperability standard, IEC 62684
- Full featured protection includes
  - Single fault
  - Output over-voltage and short-circuit
  - Input under-voltage
- Convenient SOT23-6 surface mount package for small size and low cost manufacture



C2173  
SOT23-6

### APPLICATIONS

Universal input mobile phones chargers typically to 8 W, including “universal” USB and all major OEM specifications.

Universal input adapters and standby/auxiliary power supplies typically to 8 W.

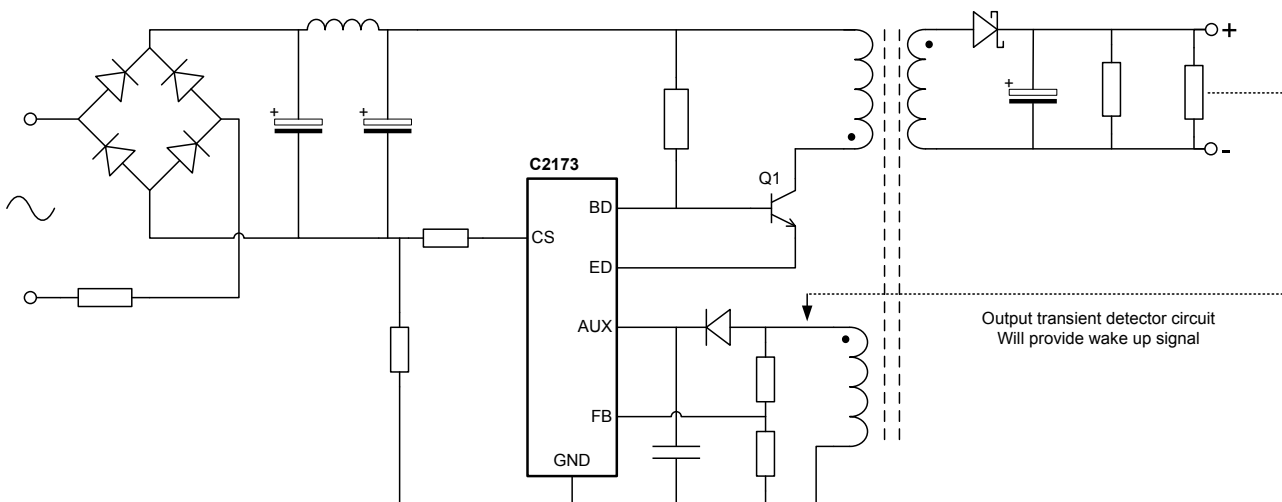


Figure 1: Typical Charger Application Circuit with C2173

### BLOCK DIAGRAM


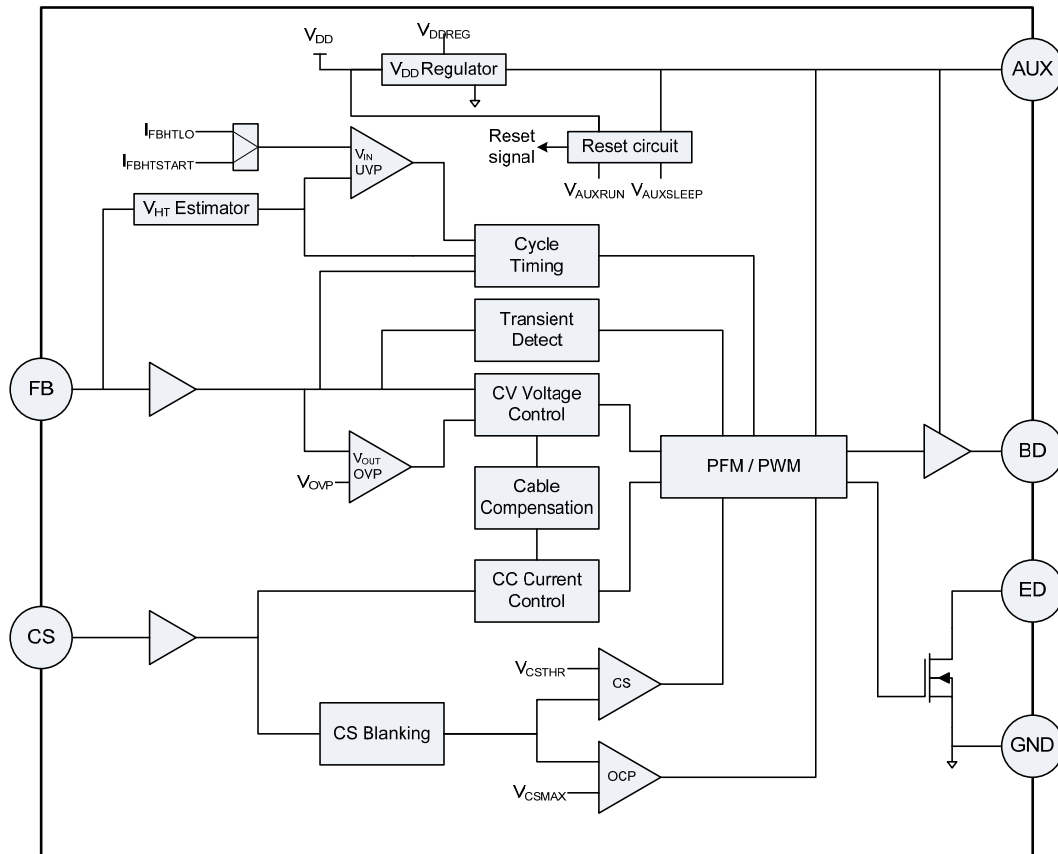


Figure 2: C2173 Block Diagram
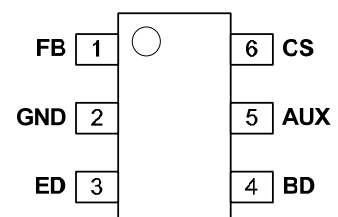
### PIN DEFINITIONS

- AUX** During Run mode, power derived from the transformer auxiliary winding is fed to the control circuitry via the AUX pin.
- BD** Base drive for BJT.
- ED** Emitter drive for BJT.
- FB** The FB input provides feedback to the control circuitry by monitoring the transformer voltage waveform, and is the input for the transient detect signal.
- GND** Power and signal ground.
- CS** Primary current sense, via Rcs.



### TYPICAL APPLICATION

Parameter	Symbol	Range or Value	Units	Comment
Supply voltage	$V_{IN}$	90 - 264	Vac	Universal mains
Output voltage	$V_{OUTCV}$	$5 \pm 5\%$	V	Constant voltage (CV) mode, at the load
Output current	$I_{OUTCC}$	$1.6 + 10\%$	A	Constant current (CC) mode
Switching frequency at full load	$f_{MAX}$	65	kHz	Determined by the chosen variant
Cable compensation	$G_{CAB}$	4	%	Determined by the chosen variant
No-load power	$P_{NL}$	< 30	mW	Without transient detect circuit
Average efficiency	$\eta$	> 81	%	Energy Star test method
Turn-on delay	$T_{ON}$	< 1	s	
Undershoot voltage	$V_{UNDERSHT}$	> 4	V	Load step from 0 to full load

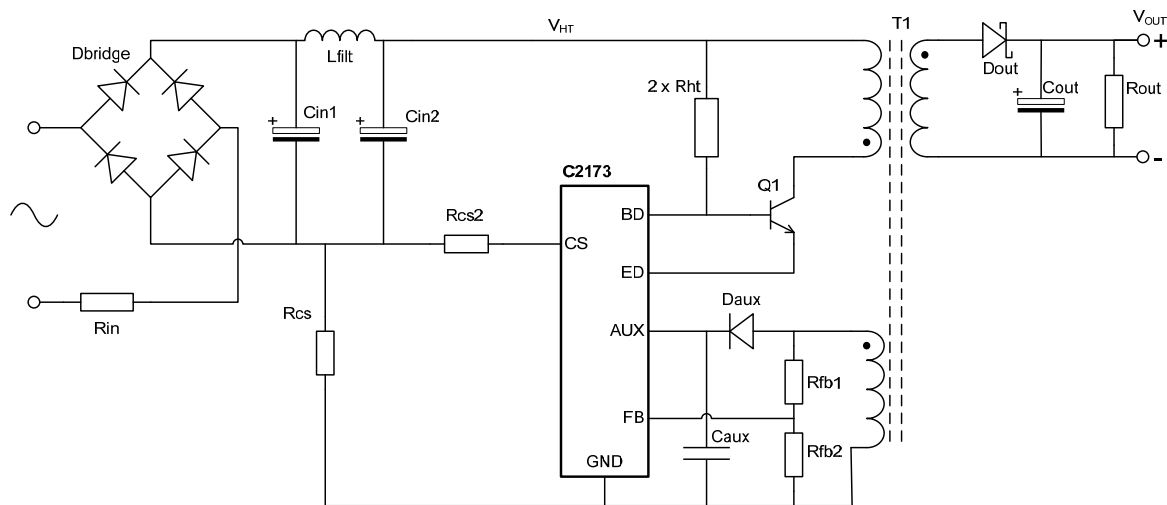


Figure 3: Typical Universal Input, 8 W Charger

By sensing the primary-side waveforms of transformer voltage and primary current, the C2173 achieves constant voltage and constant current output within tight limits without the need for any secondary-side sensing components. Figure 4 shows the output characteristics of a typical charger implementation.

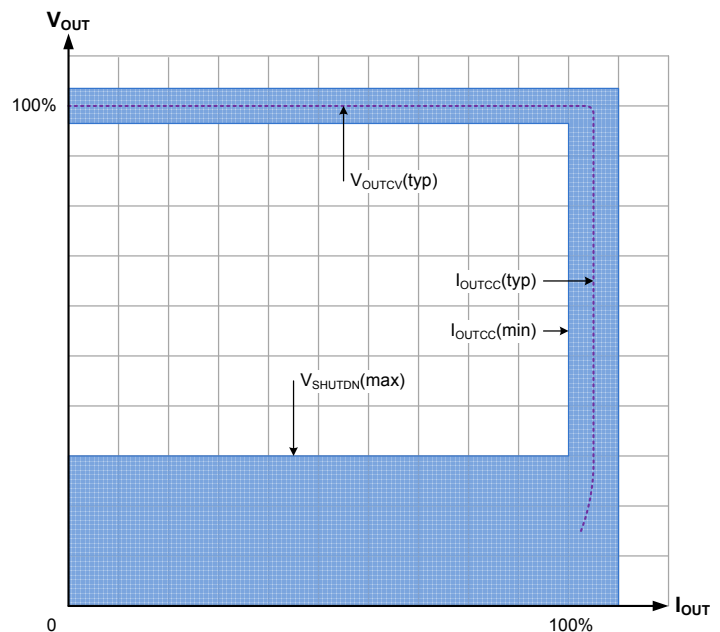


Figure 4: Typical CV/CC output characteristic achieved using C2173

### CONTACT DETAILS

Cambridge Semiconductor Ltd  
St Andrew's House  
St Andrew's Road  
Cambridge  
CB4 1DL  
United Kingdom

Phone: +44 (0)1223 446450  
Fax: +44 (0)1223 446451  
Email: [sales.enquiries@camsemi.com](mailto:sales.enquiries@camsemi.com)  
Web: [www.camsemi.com](http://www.camsemi.com)

### DISCLAIMER

The product information provided herein is believed to be accurate and is provided on an "as is" basis. Cambridge Semiconductor Ltd (CamSemi) assumes no responsibility or liability for the direct or indirect consequences of use of the information in respect of any infringement of patents or other rights of third parties. Cambridge Semiconductor Ltd does not grant any licence under its patent or intellectual property rights or the rights of other parties.

Any application circuits described herein are for illustrative purposes only. In respect of any application of the product described herein Cambridge Semiconductor Ltd expressly disclaims all warranties of any kind, whether express or implied, including, but not limited to, the implied warranties of merchantability, fitness for a particular purpose and non-infringement of third party rights. No advice or information, whether oral or written, obtained from Cambridge Semiconductor Ltd shall create any warranty of any kind. Cambridge Semiconductor Ltd shall not be liable for any direct, indirect, incidental, special, consequential or exemplary damages, howsoever caused including but not limited to, damages for loss of profits, goodwill, use, data or other intangible losses.

The products and circuits described herein are subject to the usage conditions and end application exclusions as outlined in Cambridge Semiconductor Ltd Terms and Conditions of Sale which can be found at [www.camsemi.com/legal](http://www.camsemi.com/legal).

Cambridge Semiconductor Ltd reserves the right to change specifications without notice. To obtain the most current product information available visit [www.camsemi.com](http://www.camsemi.com) or contact us at the address shown above.