

SNVS079B -MAY 2004-REVISED AUGUST 2011

LM2601

www.ti.com

LM2601 Adapter Interface Circuit

Check for Samples: LM2601

FEATURES

- **Detects an AC-DC Adapter Suitable for Battery** Charging or an Airplane or Car Power Line Adapter that Should Not be Used for Battery Charging
- Allows the Implementation of Intelligent **Switchover Circuits for Portable Systems**
- LM2601 Shuts Down Automatically When Adapter is Removed
- Low Leakage Current from Battery When Not **Powered**
- **Drives P-Channel FETs, No Schottky Diodes** are Required
- No Reverse Inrush Current from Battery Into the Adapter Output Capacitance
- **Allows for Battery Capacity Gas-Gauge** Calibration Under System Software/Firmware Control
- **Adapter Over Current Threshold Programmable with External Resistors**
- Wide Input Range: 5V 24V
- Available in TSSOP Package

APPLICATIONS

- **Portable Computers**
- Portable IAs (Internet Appliances, Information Appliances)
- **Other Battery Powered Devices**

DESCRIPTION


The Adapter Interface Circuit (AIC) is used to sense the presence of an external power source for a portable computer. It notifies the computer if a source is present and indicates if the source is appropriate for charging battery packs inside the computer. The AIC also senses an adapter current and its direction. AIC isolates the adapter and signals the computer when peak current threshold is exceeded.

LM2601 drives P-channel FETs. No high current rated Schottky diode is required to implement an circuit. switchover adapter This significantly heat dissipation decreases additional during simultaneous fast battery charging while running a computer, particularly in Maximum Performance mode of operation

Please be aware that an important notice concerning availability, standard warranty, and use in critical applications of Texas Instruments semiconductor products and disclaimers thereto appears at the end of this data sheet. All trademarks are the property of their respective owners.



Block Diagram

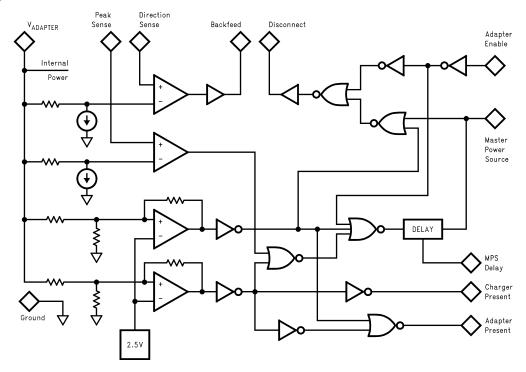

Pin Configuration

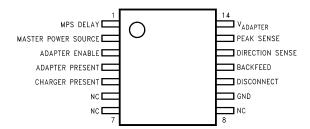


Figure 1. 14 Pin TSSOP See Package Number PW

Submit Documentation Feedback

www.ti.com

SNVS079B - MAY 2004-REVISED AUGUST 2011

PIN DESCRIPTIONS

Pin No.	Name	Function			
1	MPS DELAY	A capacitor between this pin and ground sets the delay of the MPS risetime. See MPS DELAY description in Typical Application section.			
2	MASTER POWER SOURCE	Bi-directional logic pin. If driven high by an external source, indicates that a battery is powering the power bus. If driven high by the AIC, indicates the adapter is powering the bus. AIC cannot drive MPS low. If there is no valid adapter voltage present, the pin is not an output but a high impedance logic input. The input is pulled-down via an internal 40k resistor.			
3	ADAPTER ENABLE	Logic input pin. Active high. Grants permission to the adapter to drive both the power bus and the MPS signal.			
4	ADAPTER PRESENT	Logic output pin. High when 12 volts $<$ V _{ADAPTER} $<$ 17 volts. The output typically has 40k pull-down resistor. The source current is not internally limited and the part can be damaged if the output is shorted to ground when driven HIGH.			
5	CHARGER PRESENT	Logic output pin. High when $V_{ADAPTER} > 17$ volts. The output typically has 40k pull-down resistor. The source current is not internally limited and the part can be damaged if the output is shorted to ground when driven HIGH.			
9	GND	IC ground pin.			
10	DISCONNECT	Drives the gate of the disconnect P-ch FET.			
11	BACKFEED	Drives the gate of the backfeed P-ch FET.			
12	DIRECTION SENSE	Connection for current sense resistor to control BACKFEED.			
13	PEAK SENSE	Connection for current sense resistor to control DISCONNECT.			
14	V _{ADAPTER}	Power input pin. Output of AC adapter, auto adapter or airline adapter.			



These devices have limited built-in ESD protection. The leads should be shorted together or the device placed in conductive foam during storage or handling to prevent electrostatic damage to the MOS gates.

Absolute Maximum Ratings(1)(2)

V _{ADAPTER}	-0.3V to 28V					
VPEAK SENSE, VDIRECTION SENSE, VBACI	−0.3V to V _{ADAPTER}					
VADAPTER ENABLE, VMASTER POWER SOURCE	-0.3V to 5.5V					
V _{MPS DELAY}	-0.3V to 2V					
Storage Temperature	-40°C to 125°C					
ESD Ratings	Human Body Model (3)	2kV				
	Machine Model (4)	200V				

- (1) Absolute Maximum Ratings indicate limits beyond which damage to the device may occur. Operating Ratings indicate conditions for which the device is intended to be functional, but do not ensure specific performance limits. For ensured specifications and test conditions, see the Electrical Characteristics.
- (2) If Military/Aerospace specified devices are required, please contact the Texas Instruments Sales Office/ Distributors for availability and specifications.
- (3) The human body model is a 100pF capacitor discharged through a 1.5k Ω resistor into each pin.
- (4) The machine model is a 200pF capacitor discharged directly into each pin. All pins are rated for 200V except pins 4 and 5 which are rated for 100V.

Operating Ratings⁽¹⁾

Supply Voltage (V _{ADAPTER})	5V to 24V		
Ambient Temp. Range	-20°C to 70°C		
Junction Temp. Range	−20°C to 85°C		

(1) Absolute Maximum Ratings indicate limits beyond which damage to the device may occur. Operating Ratings indicate conditions for which the device is intended to be functional, but do not ensure specific performance limits. For ensured specifications and test conditions, see the Electrical Characteristics.

Product Folder Links: LM2601

SNVS079B -MAY 2004-REVISED AUGUST 2011



Electrical Characteristics

Limits with standard typeface apply for $T_J = 25^{\circ}$ C, and limits in **boldface type** apply over the full temperature range⁽¹⁾


Symbol	Parameter	Conditions	Min	Тур	Max	Units
V_{AE}	Adapter Enable - 3V- or 5V-CMOS or TTL Logic Input	High Low	2.0		0.8	V
$V_{AP,\;CP}$	Logic Output Voltage Adapter present, Charger present	High Low, I _{SINK} = 5μA	2.9	3.1 0.25	0.6	V
V_{MPS_1}	Master Power Source 5V-CMOS Logic Input	High Low	4.0		0.8	V
V_{MPS0}	Logic Output Voltage Master Power Source	V _{ADAPTER} > 5.8V High Low	4.5	4.75 0.05	0.5	V
$V_{ADAPTER}$	Adapter Voltage for V _{AP} Low-to-High Transition		11.7	12.0	12.3	V
	Hysteresis		1.8	2.0	2.2	
V _{CHARGER}	Adapter Voltage for V _{CP} Low-to-High Transition		16.5	17.0	17.4	V
	Hysteresis		0.08	0.10	0.12	
$\Delta V_{BACKFEED}$	Current Sense Differential Voltage Threshold for Driving Backfeed FET	Vadapter - Direction sense, V _{ADAPTER} = 5V	4 3	9	17 18	mV
ΔV _{DISCONNECT}	Current Sense Differential Voltage Threshold for Driving Disconnect FET	Vadapter - Peak sense, V _{ADAPTER} = 24V	127 125	135	143 145	mV
$V_{BACKFEED}$,	FET Control Voltage	V _{ADAPTER} > 11V High		V _{ADAPTER} - 0.5V		
V _{DISCONNECT}		V _{ADAPTER} > 11V Low		V _{ADAPTER} - 10V or GND+0.5V, whichever is greater		V
t _{DRIVE}	Rise/Fall Time of FET Drive ⁽²⁾	V _{ADAPTER} = 10V C _{Load} = 3000pF		3	6	μS
IQ	Quiescent Current	V _{ADAPTER} = 24V		2	10	mA
I _{L,B} , I _{L,D}	Leakage Current into Backfeed or Disconnect	V _{ADAPTER} = 0V V _{BACKFEED} , V _{DISCONNECT} = 18V		1	15	μA
$I_{L,AE}$	Input Current into Adapter Enable Input	V _{AE} = 3.3V, Backfeed/Disconnect = 18V		50		μA
I _{L, MPS}	Input Current into MPS Input	V _{MPS} = 5.5V		175		μA
TC _{DELAY} Delay Time Temperature Coefficient				4000		ppm/°C

Submit Documentation Feedback

 ⁽¹⁾ Datasheet min/max specification limits are specified by design, test, or statistical analysis.
(2) Adapter Enable input is used to change the state of Disconnect, Direction Sense input is used to change the state of Backfeed.a. Fall time is measured as the time it takes Backfeed or Disconnect voltage to go from a high level (approx. V_{ADAPTER} – 0.5V) to (V_{ADAPTER} – 4V) after the signal is initiated at Adapter Enable or Direction Sense.b. Rise time is measured as the time it takes Backfeed or Disconnect voltage to go from a low level (approx. 0.5V) to (V_{ADAPTER} - 2V) after the signal is initiated at Adapter Enable or Direction Sense.

www.ti.com

Typical Application

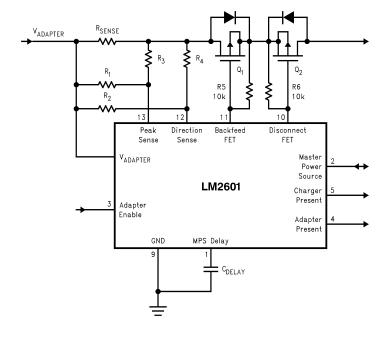

Notes

- 1. R_{SENSE} value should be selected to ensure that a programmed over current will cause a voltage drop across R_{SENSE} of approx. 135mV. If a higher value of R_{SENSE} has to be selected then R1/R3 resistor divider should be used to scale the voltage drop down.
- 2. Internal and external circuits associated with Direction Sense and Backfeed FET pins allow to emulate a Schottky diode functionality with much lower forward voltage drop and, therefore, with much lower power dissipation. R2/R4 resistor divider programs the backfeed current protection threshold. The backfeed FET Q1 turns off when the backfeed current pulse level causes more than 9 mV (typical value) voltage drop between V_{adapter} pin and Direction Sense pin.
- 3. Voltage difference (V_{DIRECTION SENSE} V_{ADAPTER}) must be higher than 20mV to reliably isolate the adapter in case of leakage.
- 4. R5 and R6 prevent the FETs from turning on unless driven by LM2601.
- 5. C_{DELAY} value can be calculated from the following formula:
 - $C_{DELAY}(nF) = T_{DELAY}(\mu s)/90$ at 25°C

Copyright © 2004-2011, Texas Instruments Incorporated

- 6. T_{DELAY} temperature coefficient equals 4000ppm/°C. See also the Figure 2 graph.
- 7. Pin Master Power Source (MPS) should be connected to System Management Controller's (SMC) and battery packs' GPIOs. When SMC detects a powered AC adapter via active signals at Charger Present or Adapter Present outputs, it asserts Adapter Enable signal and isolates the battery pack(s). Adapter Enable signal turns the Disconnect FET on. When the AC adapter is unplugged or powered off, SMC enables one of the system battery packs. The battery packs' embedded controller starts driving the logic MPS signal high that turns the Disconnect FET off.

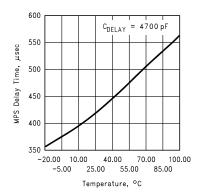


Figure 2. Typical Delay Time vs. Temperature

APPLICATION INFORMATION

The adapter interface circuit (AIC) IC provides the control functions necessary for use in mating a constant voltage output AC-DC adapter or airline adapter to a notebook computer system or a portable device. It allows optimal battery charging during computer operation, and allows battery discharge for battery gas gauge calibration. It receives control signals from the notebook computer, monitors input current from the adapter, provides adapter voltage status to the notebook system management microcontroller (or "embedded controller"), and appropriately drives MOSFET switches to electrically connect the adapter to the computer.

AIC will allow a system designer to solve various power management tasks typical for an adapter powered systems containing a rechargeable battery.

When a notebook computer is being powered from a battery and the adapter is plugged in, the computer should start drawing power from the adapter, not from the battery. The most time efficient charging scenario is when a computer draws the full rated current from a constant voltage adapter. The computer uses what it needs to run, and passes all remaining power on to the battery for charging. The computer should be able to automatically refuse to charge a battery when powered from an airplane power line. It may be necessary sometimes to have a computer fully discharging the battery and then fully recharging it (for battery gas gauge calibration purposes) while being powered by an AC adapter.

AIC will also allow a computer to prevent backfeeding current into an adapter if the adapter is not powered while being plugged into the computer (some of existing adapters can draw current from the computer under this conditions for charging the AC adapter output bulk capacitance from the computer battery).

While the lowest usable adapter voltage is about 9.5V, that is $V_{ADAPTER} = 11.7V$ minus 2.2V hysteresis, AIC is operational down to $V_{ADAPTER} = 5V$. This means that AIC will not generate false readings down to $V_{ADAPTER} = 5V$. Such false readings would be MPS = HIGH, ADAPTER PRESENT = HIGH, CHARGER PRESENT = HIGH.


AIC determines usable voltage ranges by comparing $V_{ADAPTER}$ with an internal 2.5V voltage reference (see also Electrical Characteristics). AIC detects operating current limit and leakage current limit into the adapter jack by differential sensing across current sense resistor R_{SENSE} either directly or scaled down by resistor dividers R1/R3 and R2/R4.

When designing the LM2601 into a system it may be necessary to consider ESD protection requirements for the adapter jack according to your system design spec.

Submit Documentation Feedback

PW (R-PDSO-G8)

PLASTIC SMALL OUTLINE

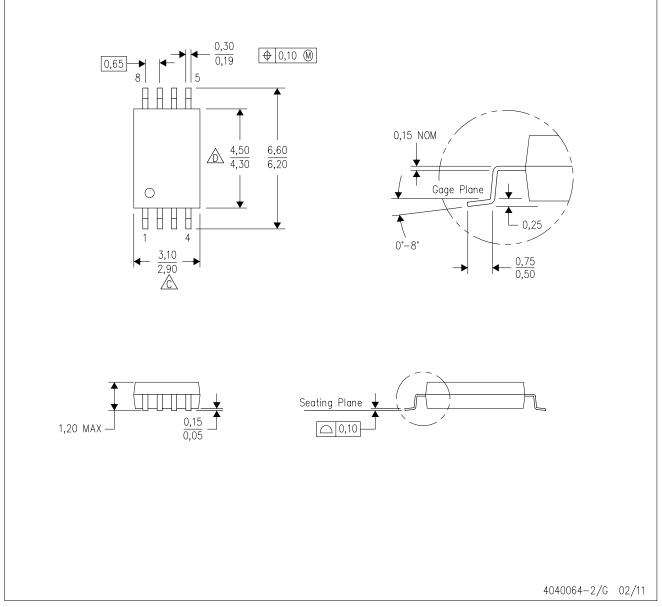

NOTES:

- A. All linear dimensions are in millimeters. Dimensioning and tolerancing per ASME Y14.5M—1994.
- B. This drawing is subject to change without notice.
- Body length does not include mold flash, protrusions, or gate burrs. Mold flash, protrusions, or gate burrs shall not exceed 0,15 each side.
- Body width does not include interlead flash. Interlead flash shall not exceed 0,25 each side.
- E. Falls within JEDEC MO-153



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have not been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products Applications

power.ti.com

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive Communications and Telecom **Amplifiers** amplifier.ti.com www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps

DSP **Energy and Lighting** dsp.ti.com www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical logic.ti.com Logic Security www.ti.com/security Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

RFID www.ti-rfid.com

Power Mgmt

OMAP Applications Processors www.ti.com/omap **TI E2E Community** e2e.ti.com

Wireless Connectivity www.ti.com/wirelessconnectivity